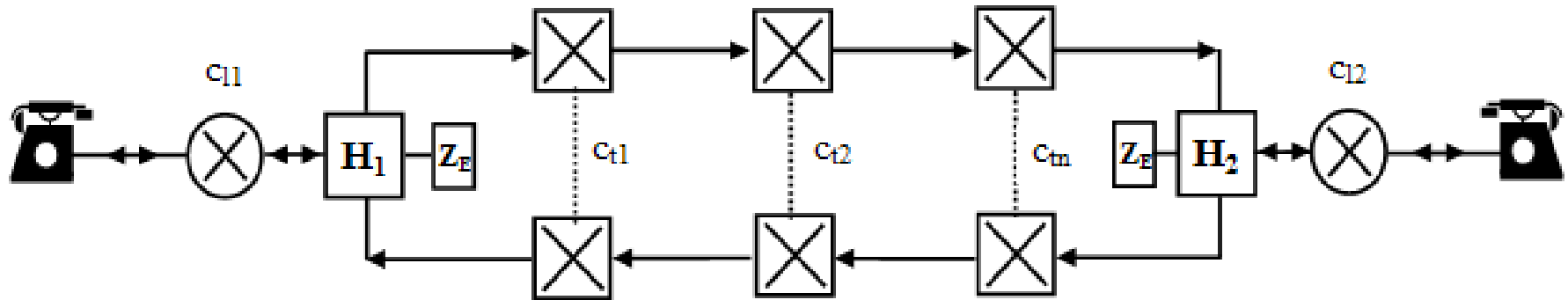


The analogue access




- The simplest access method in the telephone network;
 - it is characteristic to classical telephone networks POTS (Plain Old Telephone Service);
 - is used due to its simplicity in IDN network;
- Main characteristics of the analogue access:
 - frequency band: 300Hz – 3400Hz;
 - extended to 4kHz in digital networks;
 - two wire access and remote power supply from the exchange at -48V DC;
 - the telephone device works on four wire but the transmission to the exchange takes place on two wires;
 - the notion of four wires refers to two channels with opposite directions implemented on different physical channels (wires for example);
 - the local analogue switching takes place on two wires while the digital switching and long distance transmission (both analogue and digital) takes place on four wires.

The analogue access




- Analogue switching;

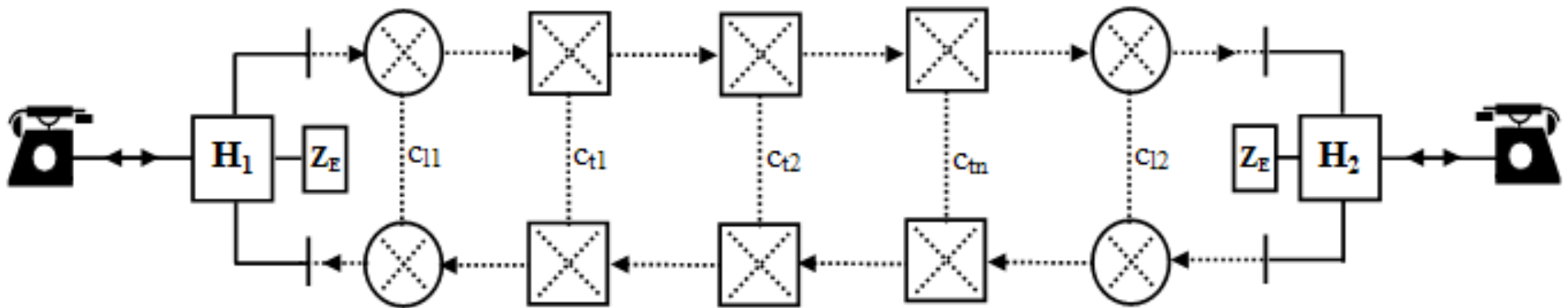

- Digital switching;
- There are necessary two 2 wire – 4 wire transition points ensured by a differential system called hybrid transformer (H);

The analogue access

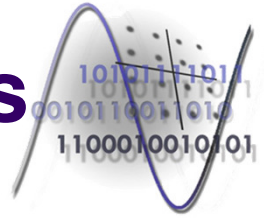


- The roles of the hybrid transformers:
 - transfers the signals generated by the terminal on the unidirectional transmission path of the 4 wire circuit;
 - transfers the signals from the transmission paths of the 4 wire circuit on the 2 wire subscriber loops;
 - attenuate the signals passing from the reception path on the transmission path of the 4 wire circuit;
 - the differential system (or hybrid transformer) represents a bridge whose balance is ensured by the relation: $Z_l = Z_b$ (or Z_E) (1), where Z_l is the line (subscriber loop) impedance, and Z_b (Z_E) is the balance impedance;
 - condition (1) cannot be fulfilled in the whole frequency band and for all subscriber loop lengths;
 - it is not ensured a perfect balance and impedance mismatch appears;
 - a fraction of the signal received from the reception path of the 4 wire loop is sent back on the transmission path of the 4 wire loop as an echo signal.


The analogue access



- Characteristics of the hybrid transformer;
 - It is called also differential system;
 - It is characteristic also to systems/equipments where is necessary a separation of the transmission and the reception paths:
 - for ex. a radio equipment using the same antenna for transmissions and reception requires a differential system to separate the output of the transmitter amplifier from the input of the receiver amplifier;
 - Represents a 4 port circuit having the following ports:
 - bidirectional port (1 – 1'):
 - ensures the connection of the 2 wire line;
 - balancing port (2 – 2'):
 - connects the balance impedance;
 - unidirectional reception port (3 – 3');
 - unidirectional transmission port (4 – 4')
 - two unidirectional ports ensuring the connection of the 4 wire line (loop).

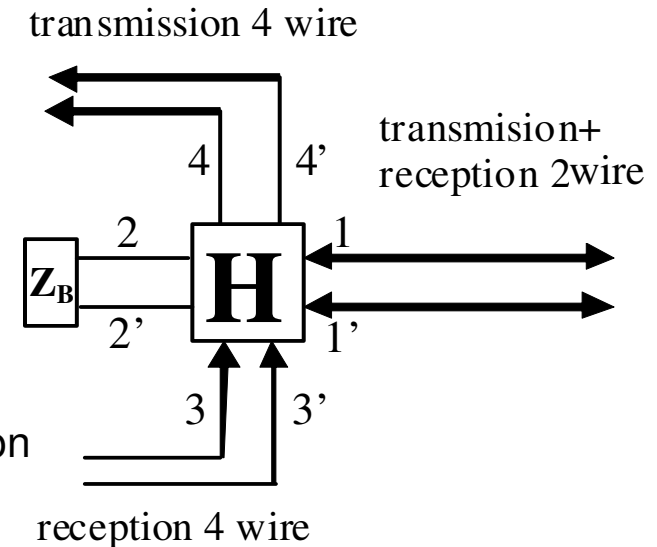


The analogue access

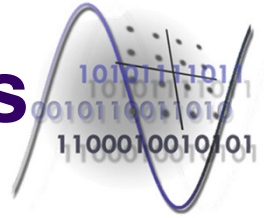


- Parameters of the hybrid transformer:
 - Attenuation between ports $(3 - 3')$ - $(4 - 4')$:
 - attenuation between the reception and transmission path of the 4 wire circuit;
 - this attenuation has to be as large as possible;
 - ideally it is an infinite attenuation and in real circuits has a value of 15 - 20dB – it is about the return loss of the hybrid transformer;
 - by reciprocity the same attenuation has to be ensured between ports $(1 - 1')$ - $(2 - 2')$, but this attenuation is not very important.
 - Attenuation between ports $(1 - 1')$ - $(4 - 4')$ and $(3 - 3')$ - $(1 - 1')$:
 - attenuation between the reception path of the 4 wire circuit and the 2 wire circuit and the attenuation between the 2 wire circuit and the transmission path of the 4 wire circuit;
 - these attenuations have to be as small as possible;
 - usually they are 3dB in the case of transformers with symmetrical structure, due to equal splitting of received/transmitted power by a port to the adjacent ports;
 - by reciprocity the attenuation between ports $(2 - 2')$ - $(4 - 4')$ is equal with attenuation between ports $(1 - 1')$ - $(4 - 4')$ and the attenuation between ports $(3 - 3')$ - $(2 - 2')$ is equal with attenuation between ports $(3 - 3')$ - $(1 - 1')$.

The analogue access

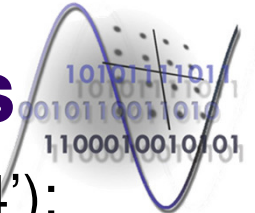


- Input / output impedances at ports (1 - 1'), (3 - 3'), (4 - 4'):
 - important from the point of view the impedance matching between the hybrid transformer and the circuits on 2 wire and 4 wire.
- Hybrid transformers from the subscriber interfaces:
 - Passive transformer with galvanic separation of circuits;
 - It is composed of two transformer with center taps.
 - It is symmetrical:
 - the symmetry depends on the symmetry of the component transformers.

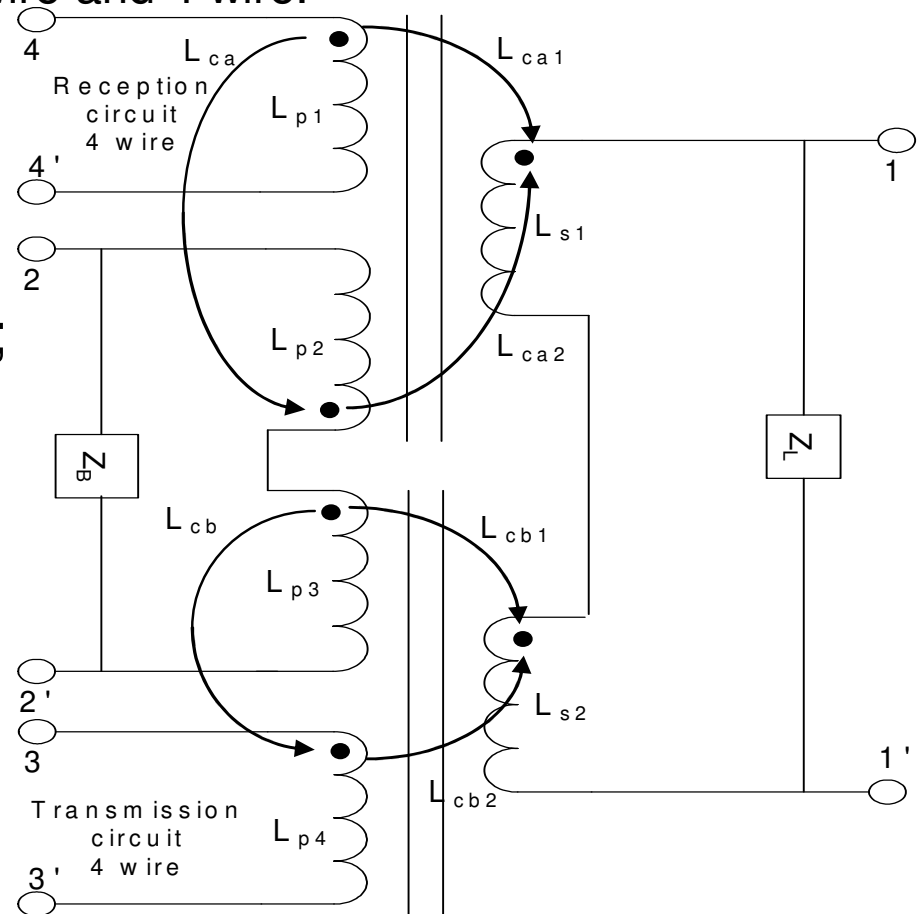


The analogue access



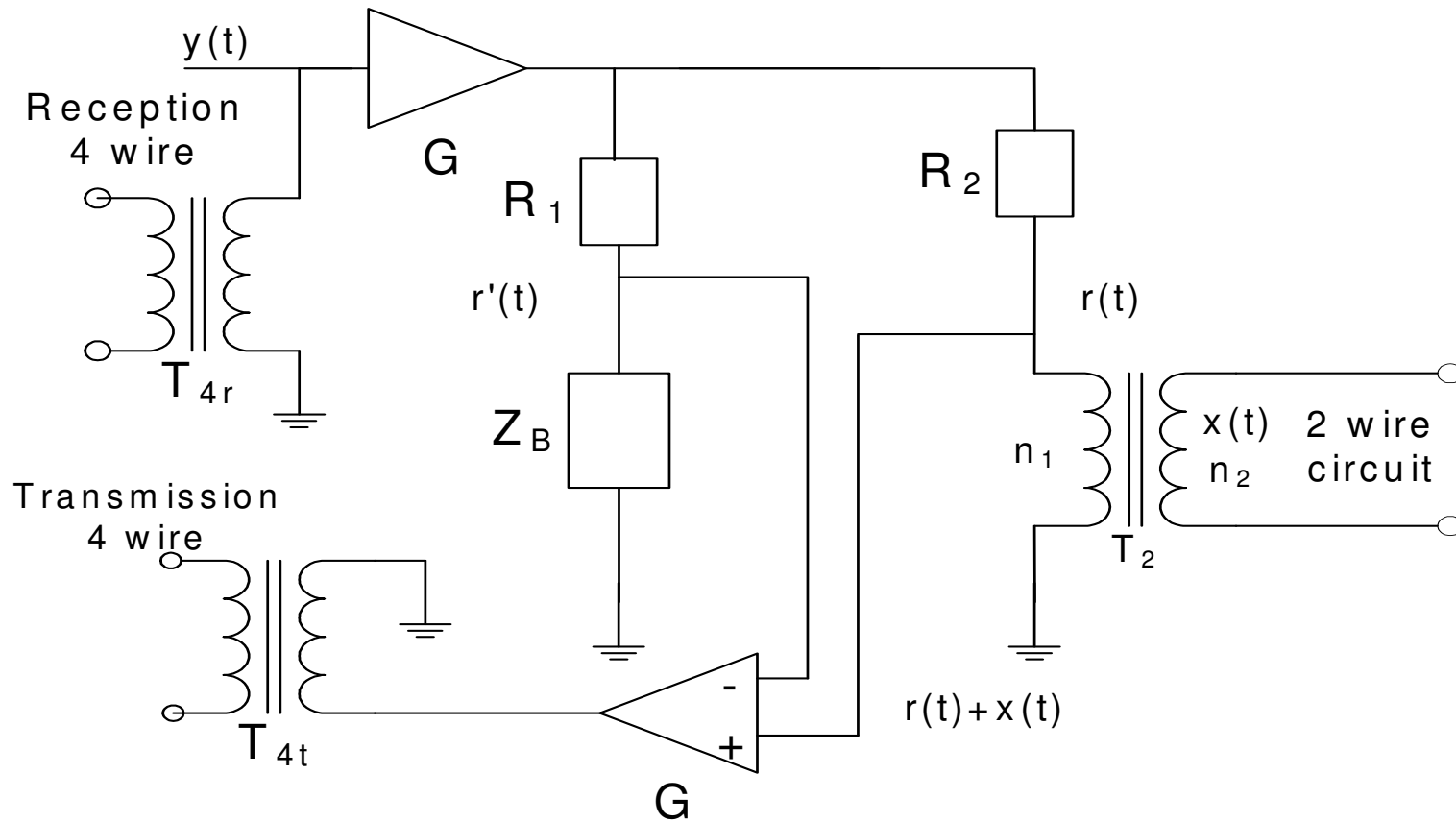- The electronic hybrid transformer;
 - The schematic of the electronic hybrid:



The analogue access

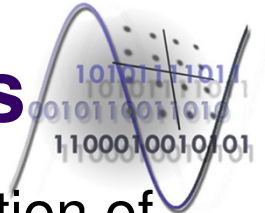

- Transformers T_{4r} , T_{4t} and T_2 ensure the galvanic separation of the hybrid from the 4 wire and 2 wire circuits;
 - ensure a symmetrical/differential character relatively to the connected circuits;
- The effective balancing bridge is composed of resistances R_1 , R_2 , impedance Z_b and impedance Z_{r-1} ;
 - Z_{r-1} is the impedance of the subscriber loop reflected in the primary winding of the transformer T_2 , and is given by:
$$Z_{r-1} = \left(\frac{n_1}{n_2} \right)^2 \cdot Z_1$$
 - Z_1 is the impedance of the 2 wire subscriber loop;
 - balance condition of the bridge:
$$\frac{R_1}{R_1 + Z_b} = \frac{R_2}{R_2 + Z_{r-1}}$$