



Course no. 9

The Theory of Electric Circuits

Technical University of Cluj-Napoca

<http://users.utcluj.ro/~lcret>

Author: Prof. Radu CIUPA

About the Course

- **Aims**
 - To provide students with an introduction to electric circuits
- **Objectives**
 - To introduce the concept of resonance in electric circuits


Topics of the course

- **Resonance in electric circuits:**
 - **Resonance in a series circuit**
 - **Resonance in a parallel circuit**
 - **Resonance in real circuits**
 - **Resonance in inductively coupled circuits**

Chapter 4

RESONANCE IN ELECTRIC CIRCUITS


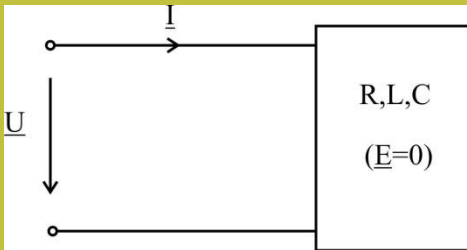
Chapter 4. Resonance in electric circuits.



- at resonance : $Q = 0$ (meaning $X = 0$ or $B = 0$)
- the phase shift between I and U is 0 ($\sin \varphi = 0$)


Remarks:

- $X = 0$ corresponds to the **series resonance**,
- $B = 0$ corresponds to **the parallel resonance**
- at resonance the current has an **extreme value**

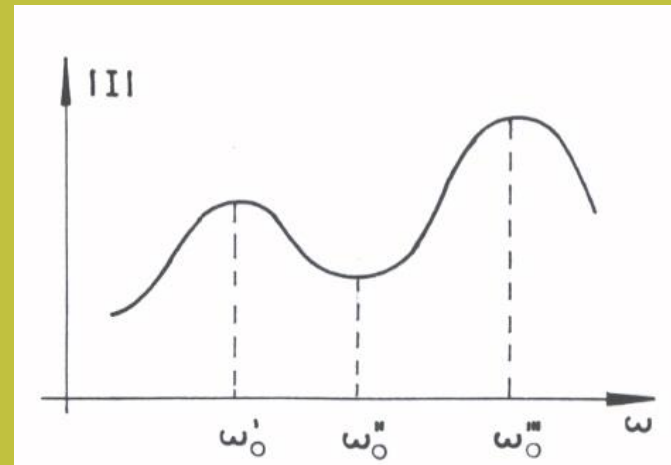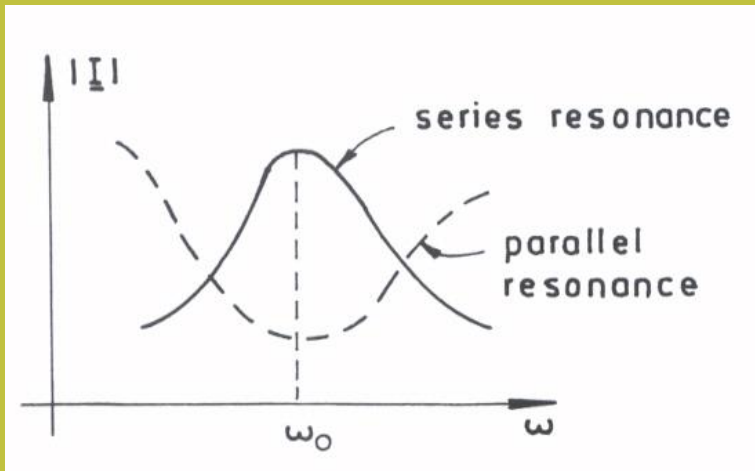

Chapter 4. Resonance in electric circuits.

4.1 RESONANCE IN A SERIES CIRCUIT.

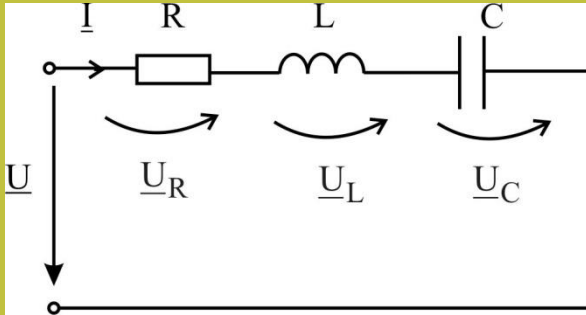

$$\underline{Z} = R + j\left(\omega L - \frac{1}{\omega C}\right)$$

$$I = \frac{U}{Z} = \frac{U}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}}$$

-The resonance condition:

$$Q = 0 \Rightarrow X = 0$$

$$\varphi = \arctg \frac{X}{R} = \arctg \frac{\omega L - \frac{1}{\omega C}}{R}$$

$$X = \omega L - \frac{1}{\omega C} = 0 \quad \text{or}$$


$$\omega L = \frac{1}{\omega C}$$

- the angular resonant frequency:

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

Chapter 4. Resonance in electric circuits.

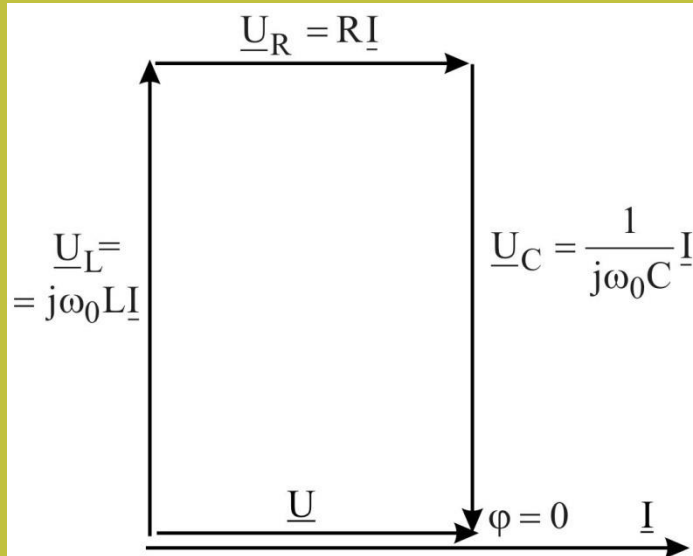The vector diagram (phasorial representation):



Remarks:

a) R does not influence the resonance.

b) $U = U_R = RI$

$$Z = \sqrt{R^2 + X^2} = R \quad \text{is minimum } (X = 0),$$

the **current is maximum**: $I = \frac{U}{R} = I_{\max}$

c) $U_L = U_C$: **voltage resonance!**

d) if $U_L = U_C \gg U \rightarrow$ **overvoltages**.

$$\frac{U_L}{U} = \frac{\omega_0 LI}{RI} = \frac{\omega_0 L}{R} > 1 \quad \text{or} \quad \omega_0 L > R, \quad \text{because} \quad \omega_0 = \frac{1}{\sqrt{LC}} \rightarrow \frac{1}{\sqrt{LC}} L = \sqrt{\frac{L}{C}} > R$$

$$\omega_0 L = \frac{1}{\omega_0 C} = \sqrt{\frac{L}{C}} = \rho$$

the characteristic impedance of a series resonant circuit

Chapter 4. Resonance in electric circuits.

$$\frac{U_L}{U} = \frac{U_C}{U} = \frac{\rho I}{RI} = \boxed{\frac{\rho}{R} = Q} \quad - \text{ the } \textit{quality factor} \text{ (or } Q\text{-factor)}$$

It shows how many times the voltage across the inductor or across the capacitance of a series resonant circuit (at resonance) is greater than the applied voltage.

$$\boxed{d = \frac{1}{Q} = \frac{R}{\rho}} \quad - \text{ the } \textit{damping factor}$$


- for the R, L, C series circuit:

$$I = \frac{U}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C} \right)^2}}$$


$$X = X_L - X_C = \omega L - \frac{1}{\omega C}$$

$$\varphi = \arctan \frac{\omega L - \frac{1}{\omega C}}{R}$$

Chapter 4. Resonance in electric circuits.

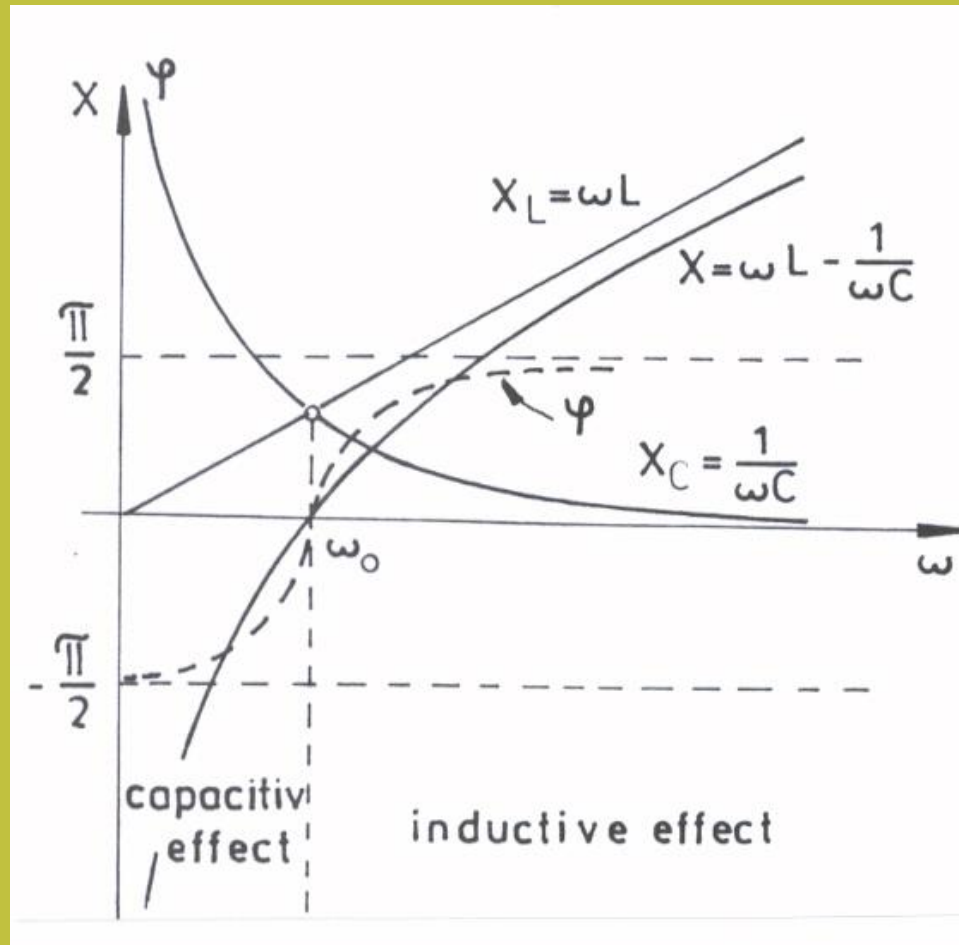

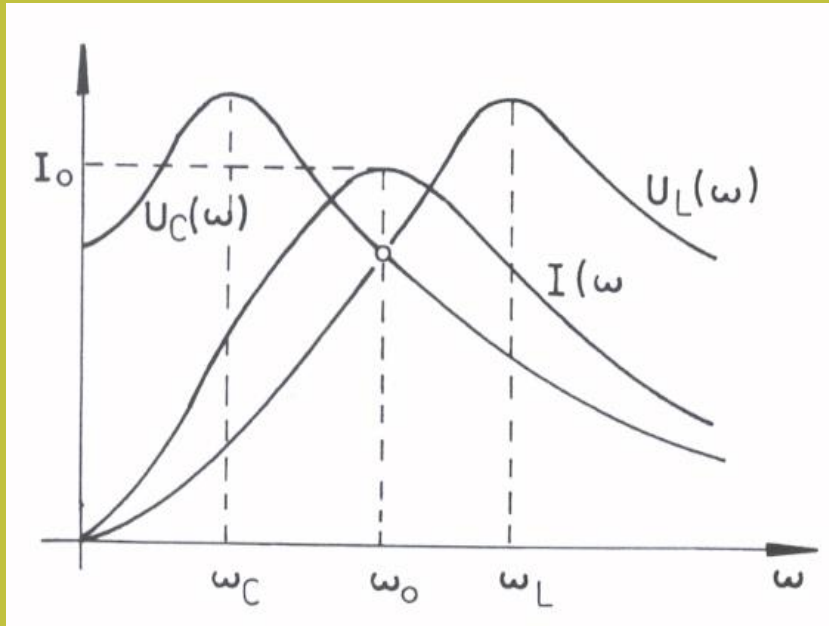Chapter 4. Resonance in electric circuits.



Note: $U_{Cmax} = U_{Lmax}$

$$U_C = \frac{1}{\omega C} I = \frac{1}{\omega C} \frac{U}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C} \right)^2}}$$

$$\frac{\partial U_C}{\partial \omega} = 0$$

$$\omega_c = \omega_0 \sqrt{\frac{2 - d^2}{2}}$$

$$U_L = \omega I = \omega L \frac{U}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C} \right)^2}}$$


$$\frac{\partial U_L}{\partial \omega} = 0$$

$$\omega_L = \omega_0 \sqrt{\frac{2}{2 - d^2}}$$

$$I_0 = \frac{U}{R}$$

$$\omega_c \leq \omega_0 \leq \omega_L$$

4.2 RESONANCE IN A PARALLEL CIRCUIT.

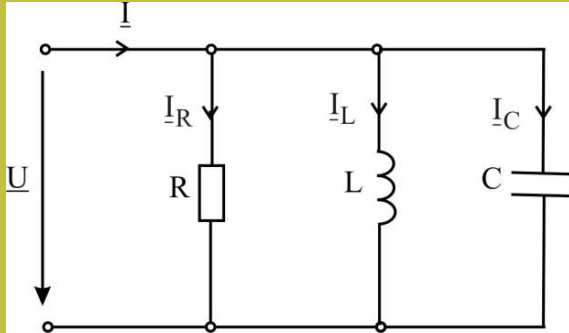

$$\underline{I} = \underline{I}_R + \underline{I}_L + \underline{I}_C$$

$$\underline{I} = \frac{\underline{U}}{R} + \frac{\underline{U}}{j\omega L} + \underline{U}j\omega C$$

$$\underline{I} = \underline{U} \left[\frac{1}{R} - j \left(\frac{1}{\omega L} - \omega C \right) \right]$$

$$\underline{I} = \underline{U}(G - jB)$$

-The resonance condition:

$$Q = 0 \Rightarrow B = 0 \quad B = \frac{1}{\omega L} - \omega C = 0$$

$$\omega L = \frac{1}{\omega C}$$


- the angular resonant frequency:

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

Remark: In practice (that is having a **real inductor** and a **real capacitor**), the resonant frequencies are **different** for the series and parallel connections.

Chapter 4. Resonance in electric circuits.

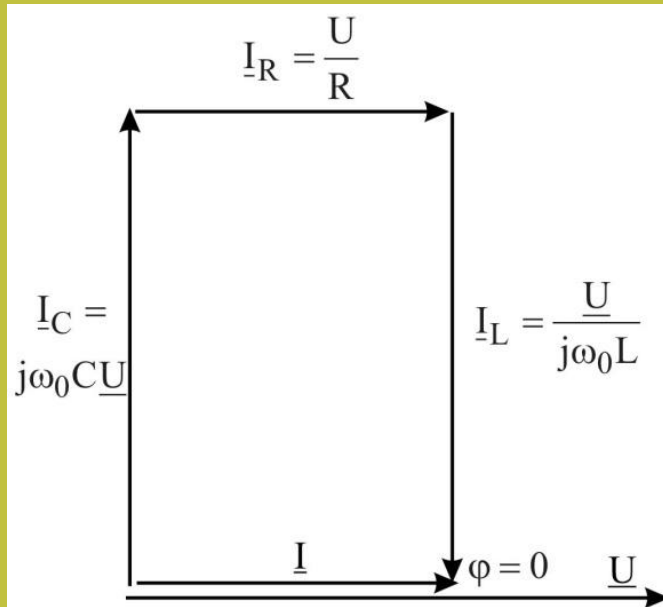The vector diagram (phasorial representation):



Remarks:

a) $I = I_R = GU = U/R$

$Y = \sqrt{G^2 + B^2} = G$ is minimum ($B = 0$),

the **current is minimum**: $I = GU = I_{\min}$

b) $I_L = I_C$: **current resonance!**

c) if $I_L = I_C \gg I$ → **overcurrents.**

$\omega_0 C = \frac{1}{\omega L} > \frac{1}{R}$ or $\omega_0 L = \frac{1}{\omega C} < R$, because $\omega_0 = \frac{1}{\sqrt{LC}}$

$\omega_0 C = \frac{1}{\omega_0 L} = \sqrt{\frac{C}{L}} = \gamma$

the characteristic admittance of a parallel resonant circuit


Chapter 4. Resonance in electric circuits.

$$Q = \frac{\gamma}{G} = \gamma R$$

- the *quality factor*

$$d = \frac{1}{Q} = \frac{G}{\gamma}$$

- the *damping factor*

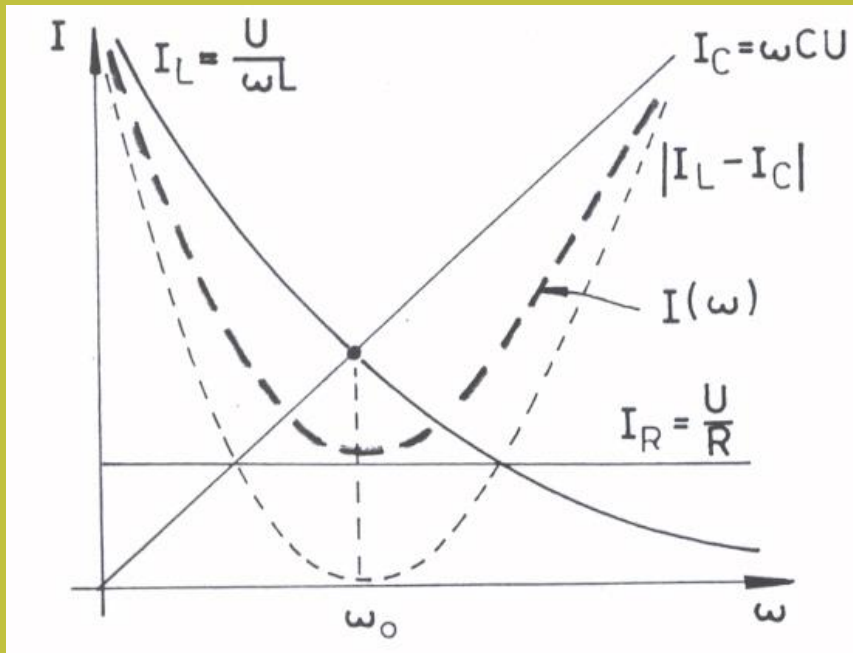

$$I_R = \frac{U}{R}$$

$$I_L = \frac{U}{\omega L}$$

$$I_C = \omega C U$$


$$\underline{I} = \underline{I}_R + \underline{I}_L + \underline{I}_C$$

$$\underline{I} = \underline{U} \left[\frac{1}{R} - j \left(\frac{1}{\omega L} - \omega C \right) \right]$$

$$I = \sqrt{I_R^2 + (I_L - I_C)^2}$$

Chapter 4. Resonance in electric circuits.

4.3 RESONANCE IN REAL CIRCUITS.

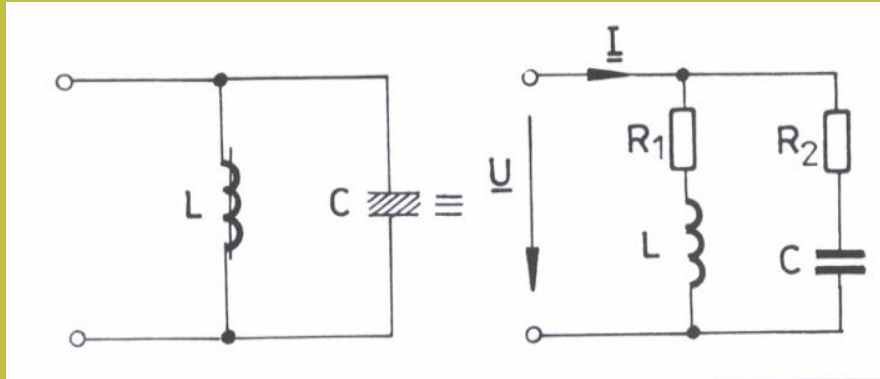

$$\underline{Z}_1 = R_1 + j\omega L \quad \text{and} \quad \underline{Z}_2 = R_2 + \frac{1}{j\omega C}$$
$$\underline{Y}_1 = \frac{1}{R_1 + j\omega L} \quad \text{and} \quad \underline{Y}_2 = \frac{1}{R_2 - \frac{j}{\omega C}}$$

$$\underline{Y}_e = \underline{Y}_1 + \underline{Y}_2 = \frac{R_1}{R_1^2 + \omega^2 L^2} + \frac{R_2}{R_2^2 + \frac{1}{\omega^2 C^2}} - j \left(\frac{\omega L}{R_1^2 + \omega^2 L^2} - \frac{\frac{1}{\omega C}}{R_2^2 + \frac{1}{\omega^2 C^2}} \right)$$

In a parallel circuit, the resonance occurs when $B_e = 0$

$$B_e = \frac{\omega L}{R_1^2 + \omega^2 L^2} - \frac{\frac{1}{\omega C}}{R_2^2 + \frac{1}{\omega^2 C^2}} = 0$$

Chapter 4. Resonance in electric circuits.

$$\omega_0 = \frac{1}{\sqrt{LC}} \sqrt{\frac{\frac{L}{C} - R_1^2}{\frac{L}{C} - R_2^2}} = \frac{1}{\sqrt{LC}} \sqrt{\frac{\rho^2 - R_1^2}{\rho^2 - R_2^2}}$$

Remarks:


- a) if $R_1 > \rho$ and $R_2 > \rho$ or $R_1 < \rho$ and $R_2 < \rho$ there is resonance;
- b) if $R_1 < \rho < R_2$ or $R_1 > \rho > R_2$ there is no resonance;
- c) if $R_1 = R_2 \neq \rho$, $\omega_0 = \frac{1}{\sqrt{LC}} \rightarrow$ the same as for a series resonant circuit
- d) if $R_1 = R_2 = \rho$, $\omega_0 = \frac{0}{0} \rightarrow$ the resonance can occur at any frequency

in this case:

$$\underline{Z}_e = \frac{\underline{Z}_1 \underline{Z}_2}{\underline{Z}_1 + \underline{Z}_2} = \frac{(R + j\omega L) \left(R - \frac{j}{\omega C} \right)}{2R + j \left(\omega L - \frac{1}{\omega C} \right)} = \rho$$

Chapter 4. Resonance in electric circuits.

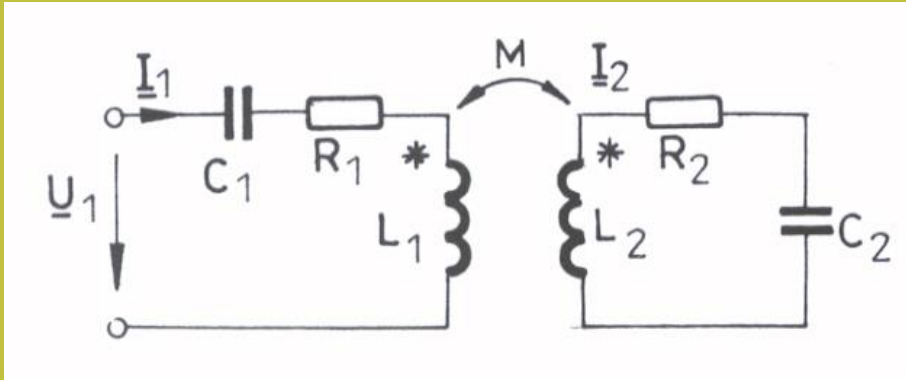4.4 RESONANCE IN INDUCTIVELY COUPLED CIRCUITS.



$$\begin{cases} \underline{U}_1 = \left[R_1 + j \left(\omega L_1 - \frac{1}{\omega C_1} \right) \right] \underline{I}_1 + j\omega M \underline{I}_2 \\ 0 = \left[R_2 + j \left(\omega L_2 - \frac{1}{\omega C_2} \right) \right] \underline{I}_2 + j\omega M \underline{I}_1 \end{cases}$$

It is possible to obtain resonance in the primary circuit, in the secondary circuit or simultaneously in both circuits.

$$\begin{cases} \frac{\underline{U}_1}{\underline{I}_1} = \underline{Z}_{e1} = R_1 + jX_1 + j\omega M \frac{\underline{I}_2}{\underline{I}_1} \\ 0 = (R_2 + jX_2) \frac{\underline{I}_2}{\underline{I}_1} + j\omega M \end{cases} \longrightarrow \frac{\underline{I}_2}{\underline{I}_1} = - \frac{j\omega M}{R_2 + jX_2}$$

where $X_1 = \omega L_1 - \frac{1}{\omega C_1}$, $X_2 = \omega L_2 - \frac{1}{\omega C_2}$

It results:

$$\underline{Z}_{e1} = R_1 + jX_1 + \frac{\omega^2 M^2}{R_2 + jX_2} = R_1 + \frac{R_2 \omega^2 M^2}{R_2^2 + X_2^2} + j \left(X_1 - \frac{\omega^2 M^2 X_2}{R_2^2 + X_2^2} \right)$$

The resonance occurs when $X_e = 0$:

$$X_1 = \frac{\omega^2 M^2 X_2}{R_2^2 + X_2^2}$$

Remarks:

- a) the resistance R_1 does not influence the resonance, while R_2 influences the resonance;
- b) the realization of the resonance of inductively coupled circuits is important especially in *radio frequencies circuits*, where we can approximate $R_2 \ll X_2$

Chapter 4. Resonance in electric circuits.

$$X_1 X_2 = \omega^2 M^2$$

$$\left(\omega L_1 - \frac{1}{\omega C_1} \right) \left(\omega L_2 - \frac{1}{\omega C_2} \right) = \omega^2 M^2$$

$$\omega^4 (1 - k^2) - \omega^2 (\omega_{01}^2 + \omega_{02}^2) + \omega_{01} \omega_{02} = 0$$


where: $k = \frac{M}{\sqrt{L_1 L_2}}$ is the coefficient of coupling,

$\omega_{01} = \frac{1}{\sqrt{L_1 C_1}}$ is the resonance frequency of the primary circuit

$\omega_{02} = \frac{1}{\sqrt{L_2 C_2}}$ is the resonance frequency of the secondary circuit

Chapter 4. Resonance in electric circuits.
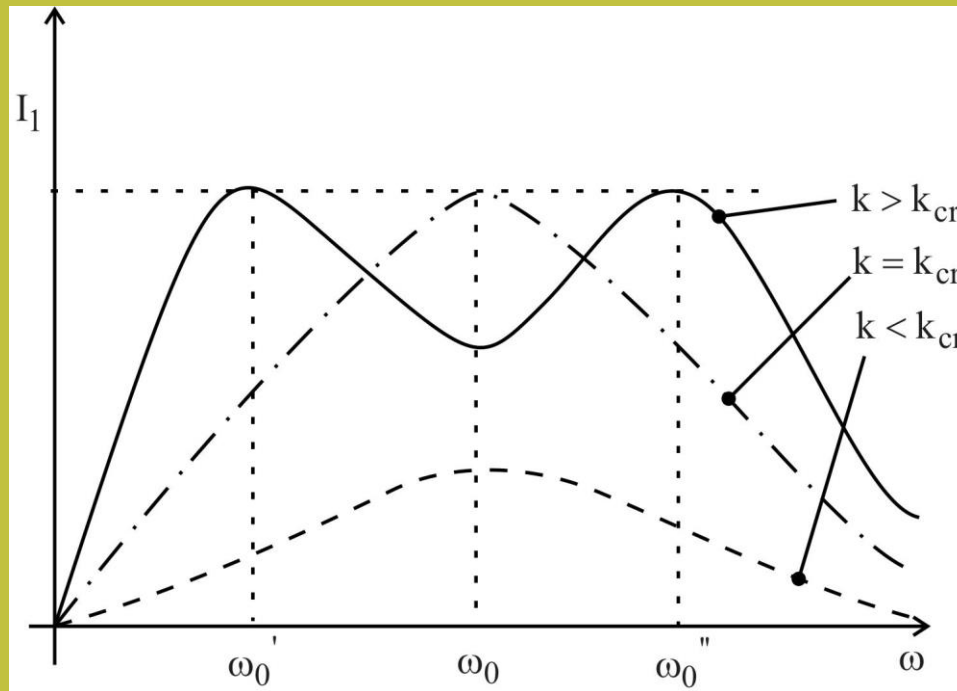
$$\omega_0', \omega_0'' = \sqrt{\frac{\omega_{01}^2 + \omega_{02}^2 \pm \sqrt{(\omega_{01}^2 + \omega_{02}^2)^2 - 4(1 - k^2)\omega_{01}^2\omega_{02}^2}}{2(1 - k^2)}}$$



$$k_{cr} = \sqrt{d^2 - \frac{d^4}{4}} \cong d \quad (\text{critical coupling})$$