

Study of the RLC serial circuit and the voltage resonance

1. Theoretical considerations

In the figure 1 is illustrated a serial circuit composed by: an ideal resistor with the resistance R , an ideal coil with the self inductance L and an ideal capacitor with the capacitance C . This circuit is supplied with sinusoidal voltage:

$$u = \sqrt{2} \cdot U \cdot \sin(\omega t + \gamma) \quad (1)$$

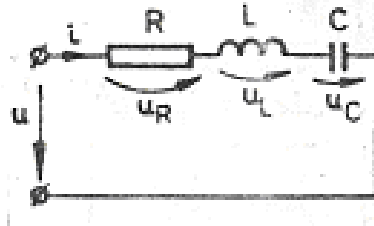


Figure 1

Applying the Ohm's law for the entire circuit we obtain the following equation:

$$u = u_R + u_L + u_C \quad (2)$$

Where

$$u_R = R \cdot i; u_L = L \frac{di}{dt}; u_C = \frac{1}{C} \int i \cdot dt \quad (3)$$

Therefore, equation (2) becomes:

$$R \cdot i + L \cdot \frac{di}{dt} + \frac{1}{C} \int i \cdot dt = \sqrt{2} U \sin(\omega t + \gamma) \quad (4)$$

We rewrite the equation (4) in complex:

$$\underline{U} = R \cdot \underline{I} + j\omega L \cdot \underline{I} + \frac{1}{j\omega C} \cdot \underline{I} = \left[R + j\left(\omega L - \frac{1}{\omega C}\right) \right] \cdot \underline{I} = (R + jX) \cdot \underline{I} \quad (5)$$

Where $X = \omega L - \frac{1}{\omega C}$ is the equivalent reactance of the circuit.

The resonance conditions for a RLC serial circuit are:

- the current i must be in phase with the voltage u ($\varphi=0$),
- the reactive power absorbed by the circuit is zero ($Q=UI \cdot \sin \varphi=0$),
- the equivalent reactance of the circuit, X , is zero:

$$X = \omega L - \frac{1}{\omega C} = 0 \quad (6)$$

From this equation, one can observe that the resonance condition can be achieved by varying the frequency ($f = \omega / 2\pi$) or the parameters L and C (the inductance L and the capacitance C).

- The resonance in a serial circuit is named the voltage resonance because at the resonance, the sum of the voltages through the coil and capacitor is zero:

$$\underline{U}_L + \underline{U}_C = j\left(\omega L - \frac{1}{\omega C}\right) \cdot \underline{I} = 0 \quad (7)$$

and their effective values can be greater than the effective value U of the voltage u .

- the current I has the maximum value at the resonance:

$$I_0 = \frac{U}{R} \quad (8)$$

- the impedance of the circuit is minimum:

$$Z = \sqrt{R^2 + X^2} \quad (9)$$

- the active power, P, is maximum.

We consider that the coil is a real coil, with the inductance L and the resistance R_L is $3,80\Omega$.

2. The Arrangement

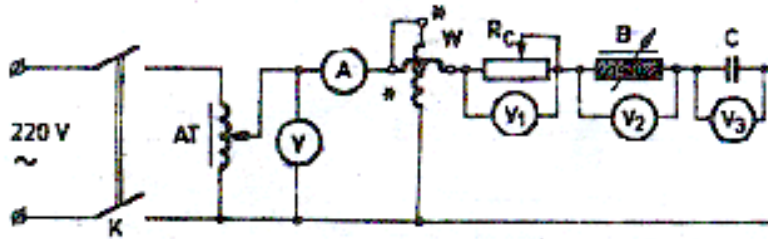


Figure 2

K - Bipolar switch

AT – Autotransformer

V, V₁, V₂, V₃ – AC current voltmeters

A – AC current ammeter

W – Wattmeter

R_C – Rheostat with cursor

B – Coil with variable inductivity

C – Capacitor

Complete table 1 with measured dates:

I [A]							
U _{RC} [V]							
U _B [V]							
U _C [V]							
P [div]							
P [W]							

3. The experimental results

$$R_C = \frac{U_{RC}}{I} - \text{Resistance of the rheostat}$$

$$R = R_C + R_L - \text{Equivalent resistance of the circuit}$$

$$\text{Total power in the circuit: } P = R \cdot I^2$$

$$R_L = \frac{P}{I^2} - R_C \text{ - Resistance of the coil}$$

$$Z_L = \frac{U_B}{I} \text{ - Impedance of the coil}$$

$$X_L = \sqrt{Z_L^2 - R_L^2} \text{ - Inductive reactance}$$

$$L = \frac{X_L}{\omega} \text{ - Inductance}$$

$$U_L = \sqrt{U_B^2 - (R_L \cdot I)^2} \text{ - Inductive voltage drop}$$

The reactance and the capacitance of the capacitor are:

$$X_C = \frac{1}{\omega C} = \frac{U_C}{I}; \quad C = \frac{10^6}{\omega X_C}$$

$$\text{The power factor of the circuit is: } \cos\varphi = \frac{P}{UI} = \frac{R_C + R_L}{\sqrt{(R_C + R_L)^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}}$$

1. Complete table 2 with the experimental results:

$R_C [\Omega]$							
$R_L [\Omega]$							
$R [\Omega]$							
$Z_L [\Omega]$							
$X_L [\Omega]$							
$L [H]$							
$U_L [V]$							
$\cos\varphi$							
$X_C [\Omega]$							
$C [\mu F]$							

2. The phase diagrams:

- before the resonance (figure 3(a))
- at the resonance (figure 3(b))
- after the resonance (figure 3(c))

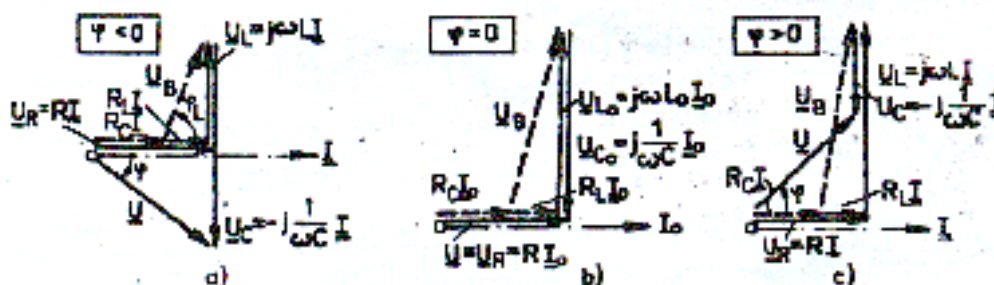


Figure 3

3. Represents the graphs for: I , P , $\cos\varphi=f(X_L)$

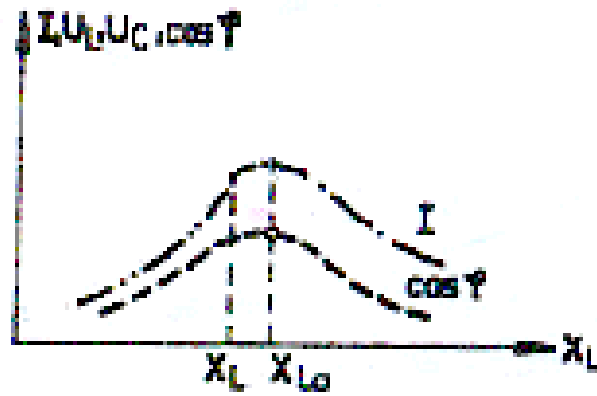


Figure 4