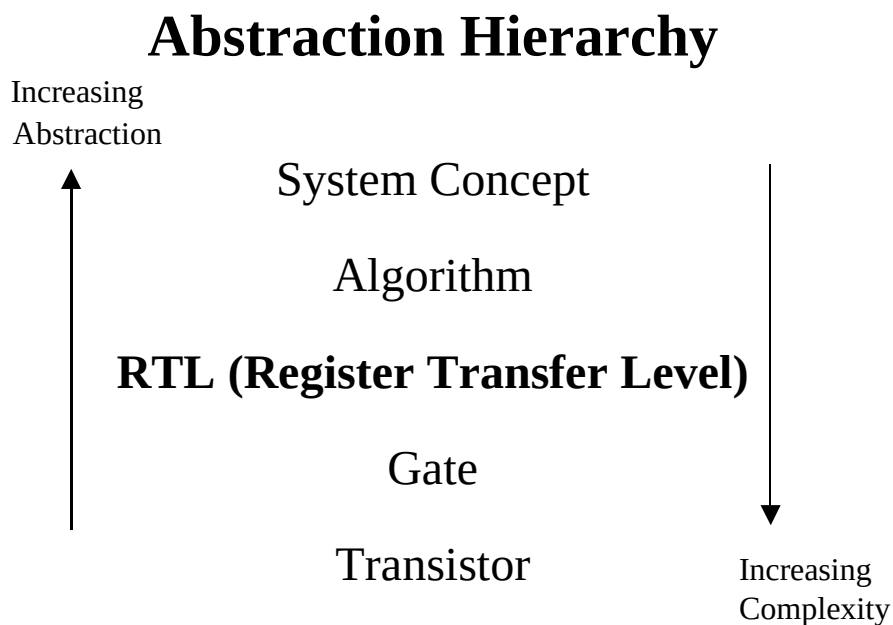


What is VHDL?

- A *hardware description language* that can be used to model a digital system.
- VHDL = VHSIC Hardware Description Language
- Very High Speed Integrated Circuit
- Can describe:
 - behaviour,
 - structure, and
 - timingof a logic circuit.

Hardware Modelling in VHDL

- VHDL is **NOT** a programming language like C or Java.
- It is used to model the physical hardware used in digital systems.
- Therefore you must always think about the hardware you wish to implement when designing systems using VHDL.



Data Objects

- A *data object* holds a value of a specified type.
- The data objects that can be synthesized directly in hardware are:
 1. **Signal:** Represents a physical wire in a circuit. It holds a list of values which includes its current value and a set of possible future values.
 2. **Variable:** Used to hold results of computations. It does not necessarily represent a wire in a circuit.
 3. **Constant:** Contains a value that cannot be changed. It is set before the beginning of a simulation.

Predefined Data Types

- Standard logic type: STD_LOGIC,
 STD_LOGIC_VECTOR
 (Can hold 0, 1, Z, and --.)
- Bit type: BIT, BIT_VECTOR
- Integer type: INTEGER
- Floating-point type: REAL
- Physical type: TIME
- Enumeration type: BOOLEAN, CHARACTER
- To use the STD_LOGIC and
STD_LOGIC_VECTOR types, the *std_logic_1164*
package must be included in the VHDL design file.
- We can define our own data types. This is
especially useful when designing finite-state machines
(FSMs).
- An object declaration is used to declare an object, its
type, its class, and optionally to assign it a value.

Object Declaration Examples

- Signal declarations:
 SIGNAL sresetn : STD_LOGIC;
 SIGNAL address : STD_LOGIC_VECTOR(7
 downto 0);
- Variable declarations:
 VARIABLE index : INTEGER range 0 to 99 :=
 20;
 VARIABLE memory : BIT_MATRIX(0 to 7, 0
 to 1023);
- Constant declarations:
 CONSTANT cycle_time : TIME := 100 ns;
 CONSTANT cst : UNSIGNED(3 downto 0);

Operators

	Operator Class	Operator
Highest Precedence	Miscellaneous	**, ABS, NOT
	Multiplication	*, /, MOD, REM
	Unary Arithmetic (Sign)	+, −
	Addition	+, −, &
	Shift/Rotate	sll, srl, sla, sra, rol, ror
Lowest Precedence	Relational	=, /=, <, <=, >, >=
	Logical	and, or, nand, nor, xor, xnor

- The individual operators in each class have the same precedence.

VHDL Design Entity

Design Entity

Entity Declaration

- Specifies the interface of entity to the outside world.
- Has a name.
- Includes PORT statement which specifies the entity's input and output signals (ports)
 - Ports can have different modes:
IN
OUT
INOUT
BUFFER


Architecture

- Provides circuit details for an entity
 - General form:
ARCHITECTURE arch_name OF entity_name IS
 Signal declarations
 Constant declarations
 Type declarations
 Component declarations
BEGIN
 Component instantiations
 Concurrent assignment statements
 Process statements
END arch_name

Concurrent Assignment Statements

- A concurrent assignment statement is used to assign a value to a signal in an architecture body.
- Used to model combinational circuits.
- The order in which these statements occur does not affect the meaning of the code.


2x4 Decoder Example

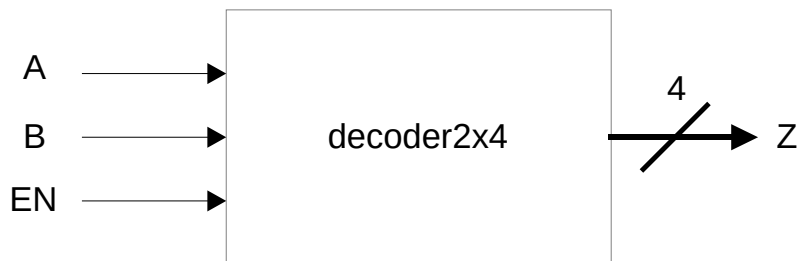

```
LIBRARY ieee;  
USE ieee.std_logic_1164.all;
```

```
ENTITY decoder2x4 IS  
    PORT (A, B, EN : IN STD_LOGIC;  
          Z : OUT STD_LOGIC_VECTOR(3 downto 0));  
END decoder2x4;  
--this is a comment
```

Architecture Body of 2x4 Decoder

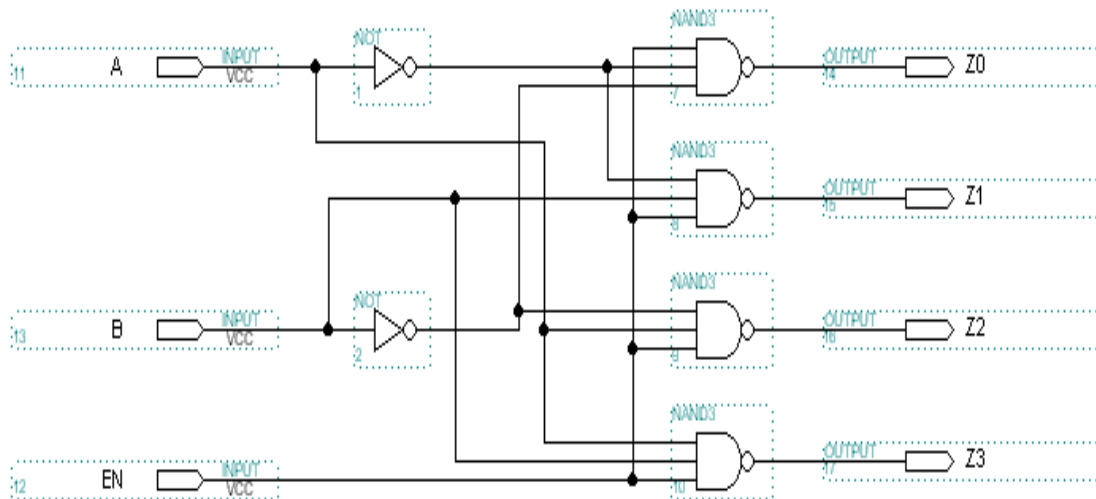

```

ARCHITECTURE dec_df OF decoder2x4 IS
    SIGNAL ABAR, BBAR : STD_LOGIC;
BEGIN
    --Order of concurrent signal assignment
    statements is not important.
    Z(3) <= not (A and B and EN);
    Z(0) <= not (ABAR and BBAR and EN);
    BBAR <= not B;
    Z(2) <= not (A and BBAR and EN);
    ABAR <= not A;
    Z(1) <= not (ABAR and B and EN);
END dec_df;
    
```

Sequential Assignment Statements

- Sequential assignment statements assign values to signals and variables. The order in which these statements appear can affect the meaning of the code.
- Can be used to model combinational circuits and sequential circuits.
- Require use of the PROCESS statement.
- Include three variants: IF statements, CASE statements, and LOOP statements.

2x4 Decoder Revisited

```
ARCHITECTURE dec_seq OF decoder2x4 IS
BEGIN
    PROCESS(A, B, EN) --Sensitivity list
        VARIABLE ABAR, BBAR : STD_LOGIC;
    BEGIN
        --Variable values assigned immediately.
        ABAR := not A;
        BBAR := not B;
        IF (EN = '1') THEN
            Z(3) <= not(A and B);
            Z(2) <= not(A and BBAR);
            Z(1) <= not(ABAR and B);
            Z(0) <= not(ABAR and BBAR);
        ELSE
            Z <= "1111";
        END IF;
    END PROCESS;
END dec_seq;
```

IF and CASE Statements

- IF and CASE statements are used to model multiplexers, decoders, encoders, and comparators.
- Can only be used in a PROCESS.

Modelling a 4–1 Multiplexer

Using an IF statement:


```
PROCESS (Sel, A, B, C, D)
BEGIN
    IF (Sel = "00") THEN
        Y <= A;
    ELSIF (Sel = "01")
    THEN
        Y <= B;
    ELSIF (Sel = "10")
    THEN
        Y <= C;
    ELSE
        Y <= D;
    END IF;
END PROCESS;
```

Using a CASE statement:

```
PROCESS (Sel, A, B, C, D)
BEGIN
    CASE Sel IS
        WHEN "00" => Y <= A;
        WHEN "01" => Y <= B;
        WHEN "10" => Y <= C;
        WHEN "11" => Y <= D;
        WHEN OTHERS => Y
        <=A;
    END CASE;
END PROCESS;
```

- Can also model multiplexers with WHEN/ELSE clause and WITH/SELECT clause. These can only be used outside of a PROCESS.

FSM Example

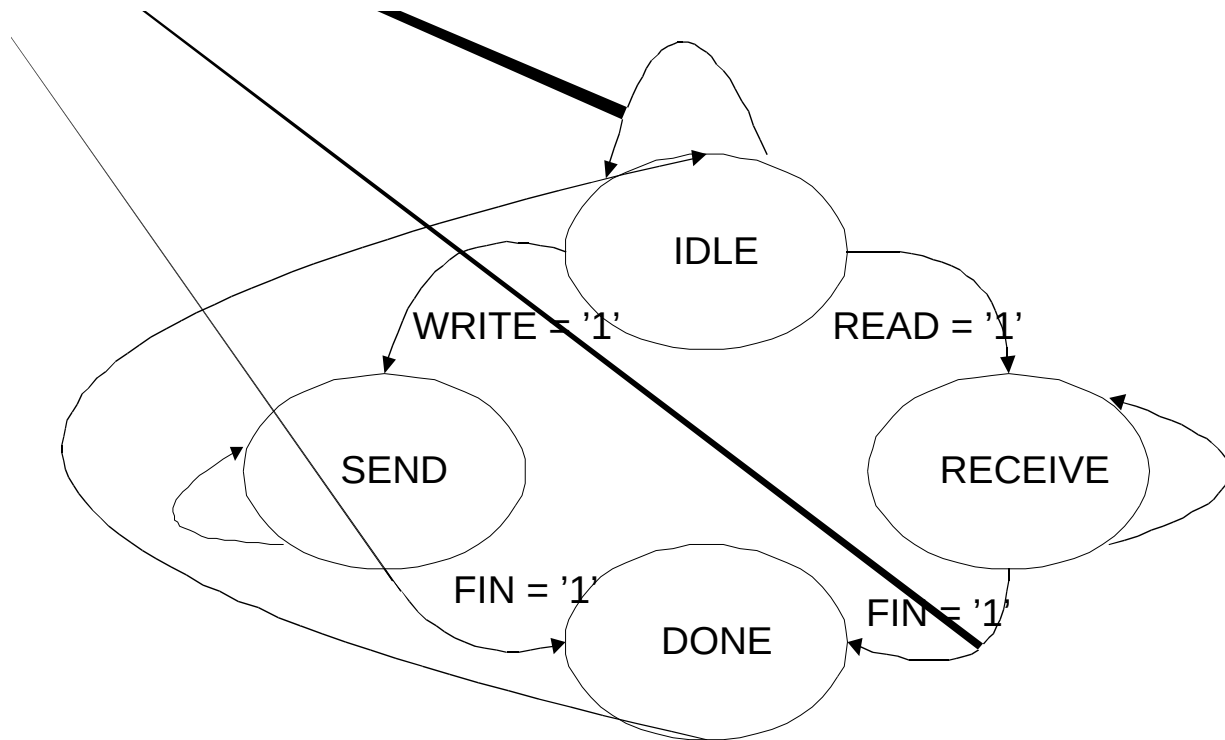


```
LIBRARY ieee;  
USE ieee.std_logic_1164.all;
```

```
ENTITY Controller IS
```

```
    PORT ( Write, Read, Fin      : IN STD_LOGIC;  
          Busy, Snd, Rec, Dn    : OUT STD_LOGIC;  
          Clock                  : IN STD_LOGIC;  
          Reset                  : IN STD_LOGIC);
```

```
END Controller;
```


FSM Example Continued

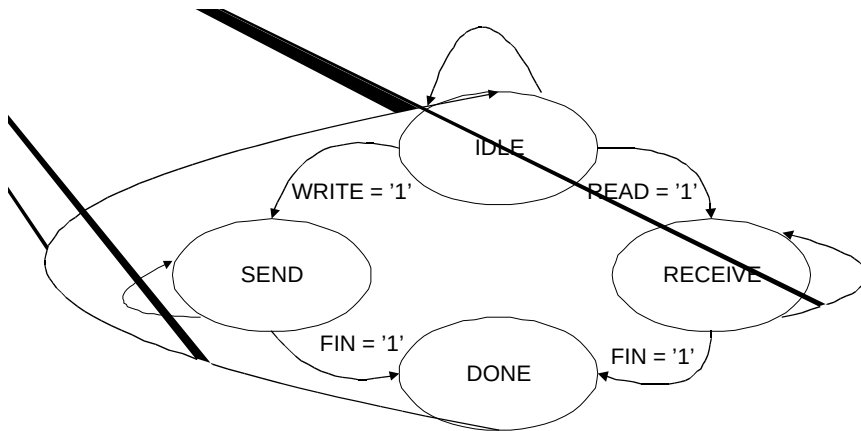

```
ARCHITECTURE My_FSM OF Controller IS
    TYPE State_Type IS (Idle, Send, Receive,
                        Done);
    SIGNAL State : State_Type;
```

```
BEGIN
    PROCESS(Reset, Clock)
    BEGIN
        IF Reset='1' THEN
            State <= Idle;
        ELSIF(Clock'EVENT and Clock='1') THEN
            CASE State IS
                WHEN Idle =>
                    IF Read='1' THEN
                        State <= Receive;
                    ELSIF Write='1' THEN
                        State <= Send;
                    ELSE
                        State <= Idle;
                    END IF;
            END CASE;
        END IF;
    END PROCESS;
```

FSM Example Continued

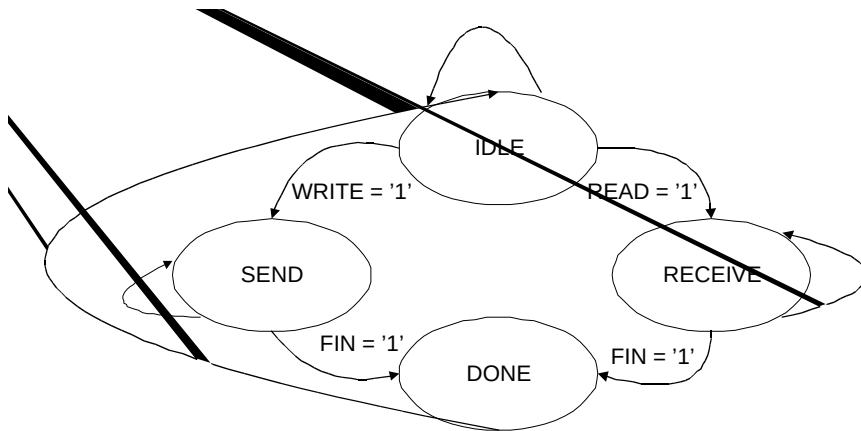

```

WHEN Receive =>
    IF Fin='1' THEN
        State <= Done;
    END IF;

```

```

WHEN Send =>
    IF Fin='1' THEN
        State <= Done;
    END IF;

```

```

        WHEN Done =>
            State <= Idle;
        END CASE;
    END IF;
END PROCESS;

```

```

Busy <= '0' WHEN State = Idle ELSE '1';
Rec  <= '1' WHEN State = Receive ELSE '0';
Snd  <= '1' WHEN State = Send ELSE '0';
Dn   <= '1' WHEN State = Done ELSE '0';

```

```


END My_FSM;

```


Behavioural vs. Structural Modelling

- With VHDL, we can describe the behaviour of simple circuit building blocks and then use these to build up the structure of a more complex circuit.
- Behavioural modelling is useful because it allows the designer to build a logic circuit without having to worry about the low-level details.
- Structural modelling is useful because it tells the synthesis tools exactly how to construct a desired circuit.

Behavioural Model of a D Flip-Flop

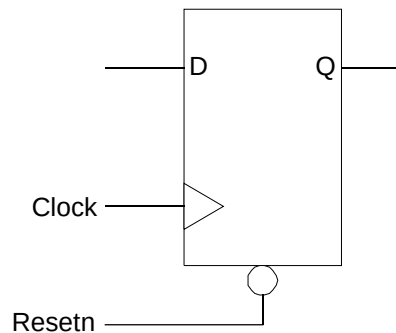

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;
```

```
ENTITY my_dff IS
    PORT ( D : IN  STD_LOGIC;
          Q : OUT STD_LOGIC;
          Clock : IN  STD_LOGIC;
          Resetn: IN  STD_LOGIC);
END my_dff;
```

```
ARCHITECTURE Behaviour OF my_dff IS
BEGIN
    PROCESS(Clock, Resetn)
    BEGIN
        IF Resetn='0' THEN
            Q <= '0';
        ELSIF (Clock'EVENT AND Clock='1') THEN
            Q <= D;
        END IF;
    END PROCESS;
END Behaviour;
```

Behavioural Model of a 4–Bit Shift Register

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;


ENTITY shift_reg_behav IS
    PORT ( Data_IN : IN STD_LOGIC;
          Data_OUT : OUT STD_LOGIC;
          Clock, Resetn : IN STD_LOGIC);
END shift_reg_behav;

ARCHITECTURE Behaviour OF shift_reg_behav IS
    SIGNAL Shift : STD_LOGIC_VECTOR(3 downto
    0);
BEGIN
    PROCESS(Clock, Resetn)
    BEGIN
        IF Resetn='0' THEN
            Shift <= "0000";
        ELSIF (Clock'EVENT AND Clock='1') THEN
            Shift(3) <= Data_IN;
            --shift data to the right
            Shift(2 downto 0) <= Shift(3 downto 1);
        END IF;
    END PROCESS;

    Data_OUT <= Shift(0);

END Behaviour;
```

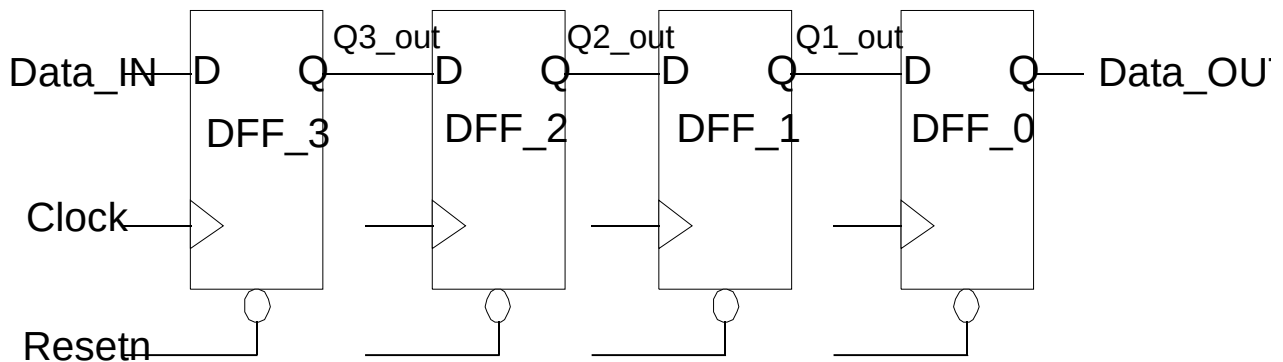Structural Model of a 4-Bit Shift Register



```
LIBRARY ieee;
```

```
USE ieee.std_logic_1164.all;
```

```
ENTITY shift_reg_struct IS
```


```
    PORT (Data_IN : IN STD_LOGIC;
```

```
          Data_OUT: OUT STD_LOGIC;
```

```
          CLK, RESN : IN STD_LOGIC);
```

```
END shift_reg_struct;
```

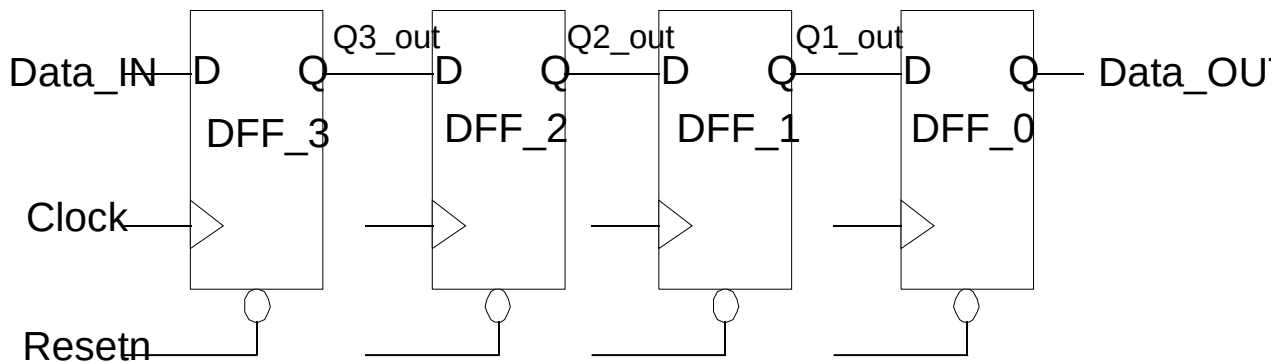Structural Model of a 4–Bit Shift Register Cont.



ARCHITECTURE Structure OF shift_reg_struct IS

COMPONENT my_dff

PORT (D : IN STD_LOGIC;
Q : OUT STD_LOGIC;
Clock : IN STD_LOGIC;
Resetn: IN STD_LOGIC);

END COMPONENT;

SIGNAL Q3_out, Q2_out, Q1_out : STD_LOGIC;

BEGIN

DFF_3 : my_dff PORT MAP (Data_IN, Q3_out, CLK, RESN);

DFF_2 : my_dff PORT MAP (Q3_out, Q2_out, CLK, RESN);

DFF_1 : my_dff PORT MAP (D=>Q2_out, Q=>Q1_out,
Clock=>CLK, Resetn=>RESN);

DFF_0 : my_dff PORT MAP (D=>Q1_out, Q=>Data_OUT,
Clock=>CLK, Resetn=>RESN);

END Structure;

Using Altera's Library of Parameterized Modules (LPMs)

- Altera MAX+plus II has numerous predefined circuit building blocks in its LPMs.
- These libraries include everything from full-adders to ROMs.

Altera LPM Flip-Flop

- Must include library and use:

```
LIBRARY lpm;
```

```
USE lpm.lpm_components.all;
```

```
COMPONENT lpm_ff
```

```
  GENERIC (LPM_WIDTH: POSITIVE;
```

```
    LPM_AVALUE: STRING := "UNUSED";
```

```
    LPM_FFTYPE: STRING := "FFTYPE_DFF";
```

```
    LPM_TYPE: STRING := "L_FF";
```

```
    LPM_SVALUE: STRING := "UNUSED";
```

```
    LPM_HINT: STRING := "UNUSED");
```

```
  PORT (data: IN STD_LOGIC_VECTOR(LPM_WIDTH-1  
    DOWNT0 0);
```

```
    clock: IN STD_LOGIC;
```

```
    enable: IN STD_LOGIC := '1';
```

```
    sload: IN STD_LOGIC := '0';
```

```
    sclr: IN STD_LOGIC := '0';
```

```
    sset: IN STD_LOGIC := '0';
```

```
    aload: IN STD_LOGIC := '0';
```

```
    aclr: IN STD_LOGIC := '0';
```

```
    aset: IN STD_LOGIC := '0';
```

```
    q: OUT STD_LOGIC_VECTOR(LPM_WIDTH-1 DOWNT0  
    0));
```

```
END COMPONENT;
```

Altera LPM Flip-Flop Device Description

Ports:

INPUTS

Port Name	Required	Description	Comments
data[]	No	T-type flipflop: Toggle enable D-type flipflop: Data input	Input port LPM_WIDTH wide. If the data[] input is not used, at least one of the aset, aclr, sset, or sclr ports must be used. Unused data inputs default to GND.
clock	Yes	Positive-edge-triggered Clock.	
enable	No	Clock Enable input.	Default = 1.
sclr	No	Synchronous Clear input.	If both sset and sclr are used and both are asserted, sclr is dominant. The sclr signal affects the output q[] values before polarity is applied to the ports.
sset	No	Synchronous set input.	Sets q outputs to the value specified by LPM_SVALUE, if that value is present, or sets the q outputs to all 1's. If both sset


OUTPUTS

Port Name	Required	Description	Comments
q[]	Yes	Data output from D or T flipflops.	Output port LPM_WIDTH wide.

Parameters:

Parameter	Type	Required	Description
LPM_WIDTH	Integer	Yes	Width of the data[] and q[] ports.
LPM_AVALUE	Integer	No	Constant value that is loaded when aset is high. If omitted, defaults to all 1's. The LPM_AVALUE parameter is limited to a maximum of 32 bits.
LPM_SVALUE	Integer	No	Constant value that is loaded on the rising edge of clock when sset is high. If omitted, defaults to all 1's.
LPM_FFTYPE	String	No	Values are "DFF", "TFF", and "UNUSED". Type of flipflop. If omitted, the default is "DFF". When the LPM_FFTYPE parameter is set to "DFF", the sload port is ignored.
LPM_HINT	String	No	Allows you to specify Altera-specific parameters in VHDL Design Files. The default is "UNUSED".
LPM_TYPE	String	No	Identifies the LPM entity name in VHDL Design Files.

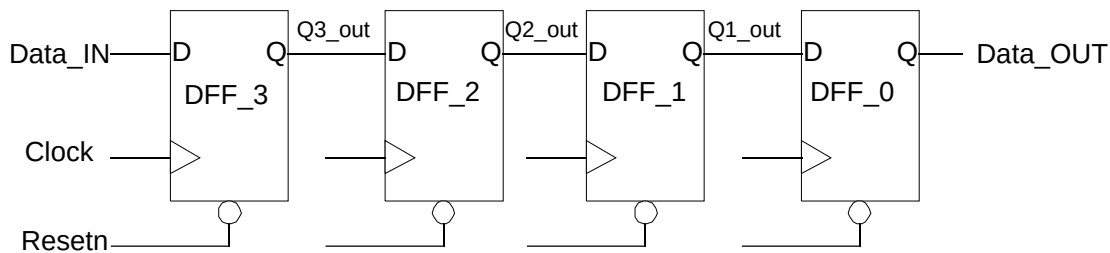Structural Description of Shift Register Using Altera's Flip-Flop LPM



```
LIBRARY ieee;  
USE ieee.std_logic_1164.all;  
LIBRARY lpm;  
USE lpm.lpm_components.all;
```

```
ENTITY shift_reg_struct2 IS
```

```
PORT (
```

```
    Data_IN : IN STD_LOGIC_VECTOR(0 downto 0);
```

```
    Data_OUT: OUT STD_LOGIC_VECTOR(0  
        downto 0);
```

```
    CLK, RESN : IN STD_LOGIC);
```

```
END shift_reg_struct2;
```


Structural Description of Shift Register Using Altera's Flip-Flop LPM Cont.

ARCHITECTURE Structure OF shift_reg_struct2 IS

SIGNAL Q3_out, Q2_out, Q1_out :

STD_LOGIC_VECTOR(0 downto 0);

SIGNAL Reset_Internal : STD_LOGIC;

BEGIN

Reset_Internal <= not RESN;

DFF_3 : lpm_ff GENERIC MAP (LPM_WIDTH=>1,
LPM_FFTYPE=>"DFF")

PORT MAP (data=>Data_IN, q=>Q3_out,
clock=>CLK, aclr=>Reset_Internal);

DFF_2 : lpm_ff GENERIC MAP (LPM_WIDTH=>1,
LPM_FFTYPE=>"DFF")

PORT MAP (data=>Q3_out, q=>Q2_out,
clock=>CLK, aclr=>Reset_Internal);

DFF_1 : lpm_ff GENERIC MAP (LPM_WIDTH=>1,
LPM_FFTYPE=>"DFF")

PORT MAP (data=>Q2_out, q=>Q1_out,
clock=>CLK, aclr=>Reset_Internal);

DFF_0 : lpm_ff GENERIC MAP (LPM_WIDTH=>1,
LPM_FFTYPE=>"DFF")

PORT MAP (data=>Q1_out, q=>Data_OUT,
clock=>CLK, aclr=>Reset_Internal);

END Structure;