

8086 - 80386SX 16-bit Memory Interface


These machines differ from the 8088/80188 in several ways:

- The data bus is *16-bits* wide.
- The $\text{IO}/\overline{\text{M}}$ pin is replaced with $\text{M}/\overline{\text{IO}}$ (8086/80186) and $\overline{\text{MRDC}}$ and $\overline{\text{MWTC}}$ for 80286 and 80386SX.
- $\overline{\text{BHE}}$, **Bus High Enable**, control signal is added.
- Address pin A_0 (or $\overline{\text{BLE}}$, **Bus Low Enable**) is used differently.

The 16-bit data bus presents a new problem:

The microprocessor must be able to read and write data to any 16-bit location in addition to any 8-bit location.

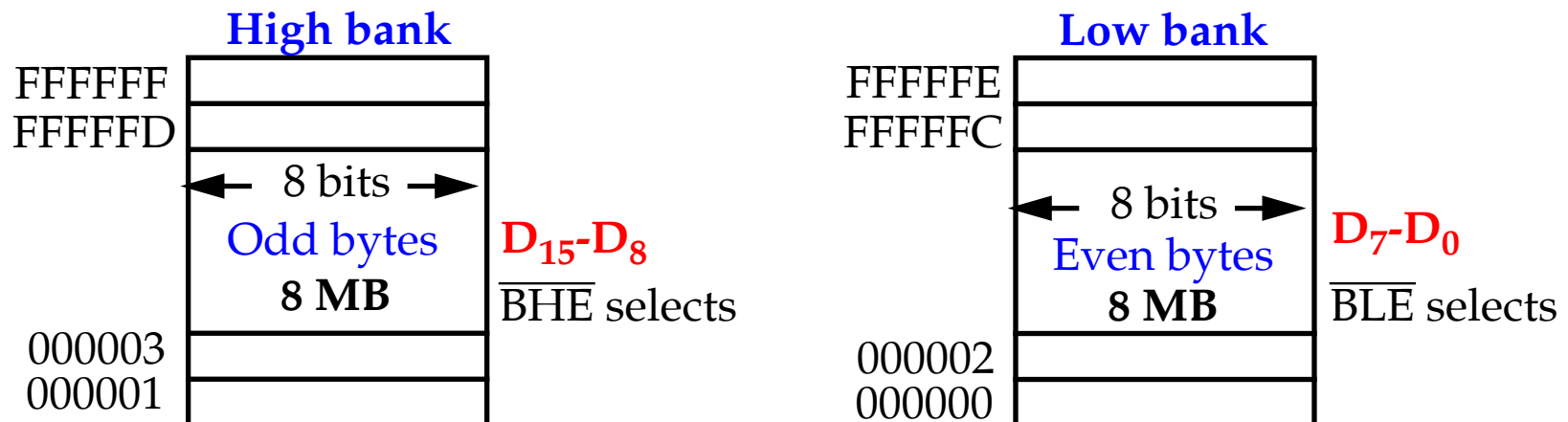The data bus and memory are divided into banks:



8086 - 80386SX 16-bit Memory Interface

BHE and BLE are used to select one or both:

| $\overline{\text{BHE}}$ | $\overline{\text{BLE}}$ | Function |
|-------------------------|-------------------------|---|
| 0 | 0 | Both banks enabled for 16-bit transfer |
| 0 | 1 | High bank enabled for an 8-bit transfer |
| 1 | 0 | Low bank enabled for an 8-bit transfer |
| 1 | 1 | No banks selected |

Bank selection can be accomplished in two ways:


- Separate write decoders for each bank (which drive $\overline{\text{CS}}$).
- A separate write signal (strobe) to each bank (which drive $\overline{\text{WE}}$).

Note that 8-bit read requests in this scheme are handled by the microprocessor (it selects the bits it wants to read from the 16-bits on the bus).

There does not seem to be a big difference between these methods although the book claims that there is.

Note in either method that A_0 does not connect to memory and bus wire A_1 connects to memory pin A_0 , A_2 to A_1 , etc.

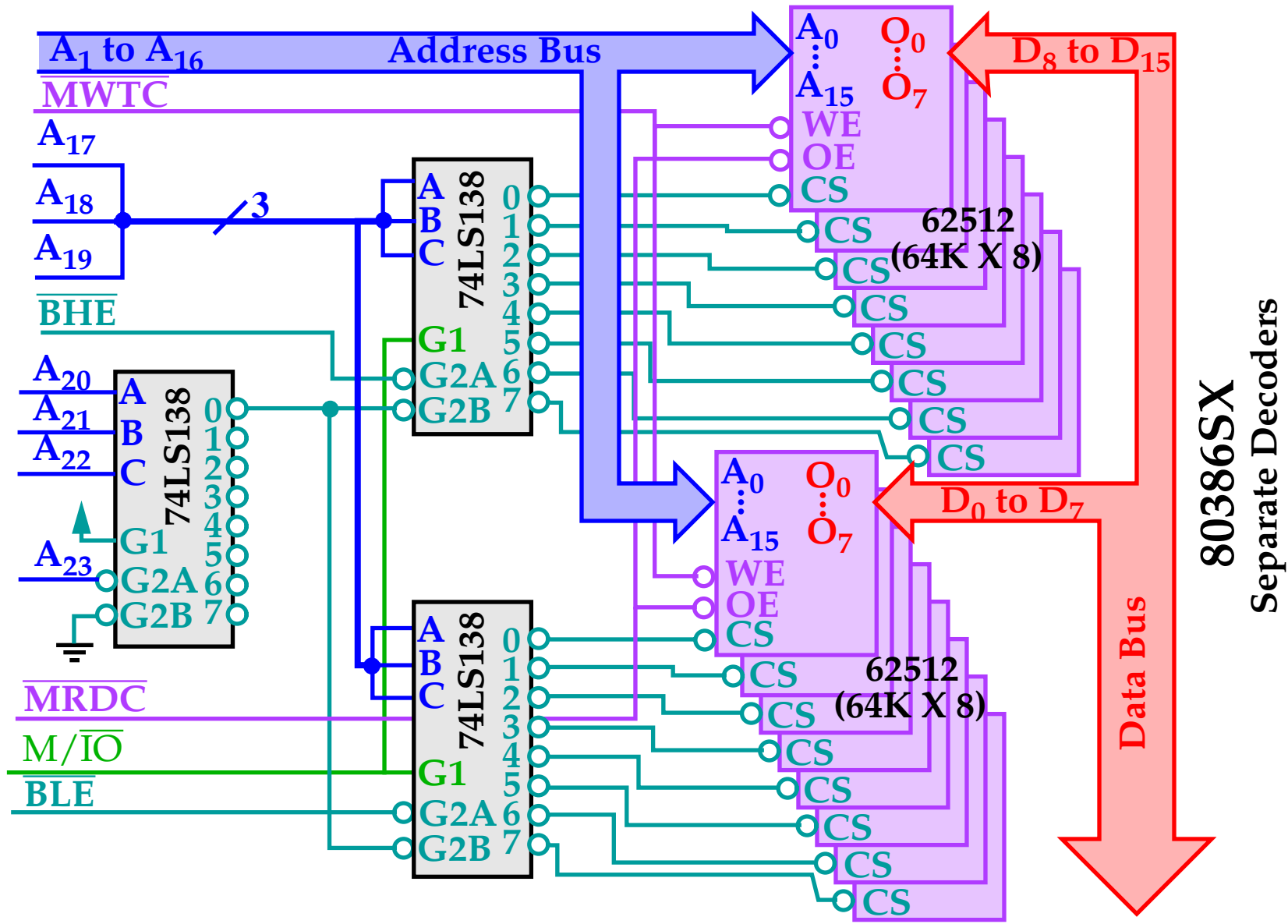80386SX 16-bit Memory Interface (Separate Decoders)



Memory Interfaces

See text for *Separate Write Strobe* scheme plus some examples of the integration of EPROM and SRAM in a complete system.

It is just an application of what we've been covering.

80386DX and 80486 have 32-bit data buses and therefore 4 banks of memory. 32-bit, 16-bit and 8-bit transfers are accomplished by different combinations of the bank selection signals $\overline{\text{BE}}_3$, $\overline{\text{BE}}_2$, $\overline{\text{BE}}_1$, $\overline{\text{BE}}_0$.

The Address bits A_0 and A_1 are used within the microprocessor to generate these signals.

They are *don't cares* in the decoding of the 32-bit address outside the chip (using a PLD such as the **PAL 16L8**).

The high clock rates of these processors usually require **wait states** for memory access.

We will come back to this later.


Pentium Memory Interface

The Pentium, Pentium Pro, Pentium II and III contain a 64-bit data bus.


Therefore, 8 decoders or 8 write strobes are needed as well as 8 memory banks.

The write strobes are obtained by combining the bank enable signals ($\overline{\text{BEx}}$) with the $\overline{\text{MWTC}}$ signal.

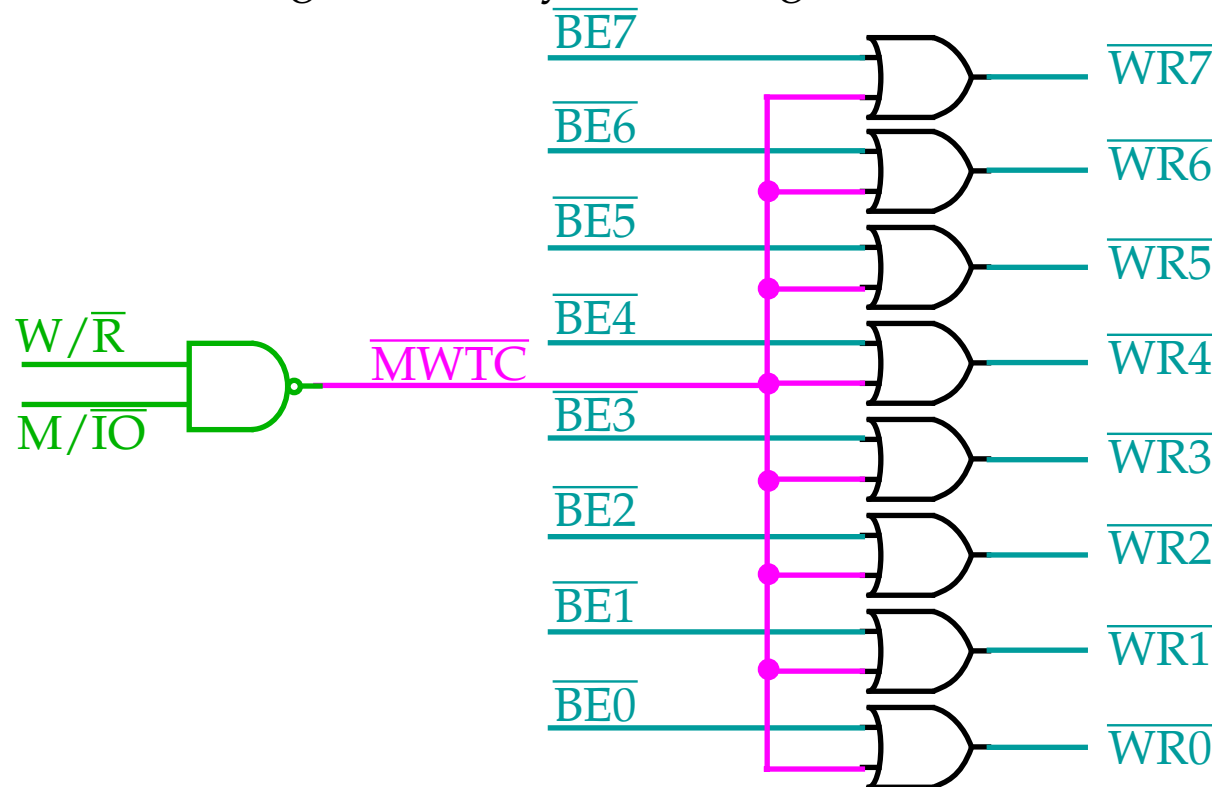$\overline{\text{MWTC}}$ is generated by combining the $\text{M}/\overline{\text{IO}}$ and $\text{W}/\overline{\text{R}}$ signals.




Pentium Memory Interface

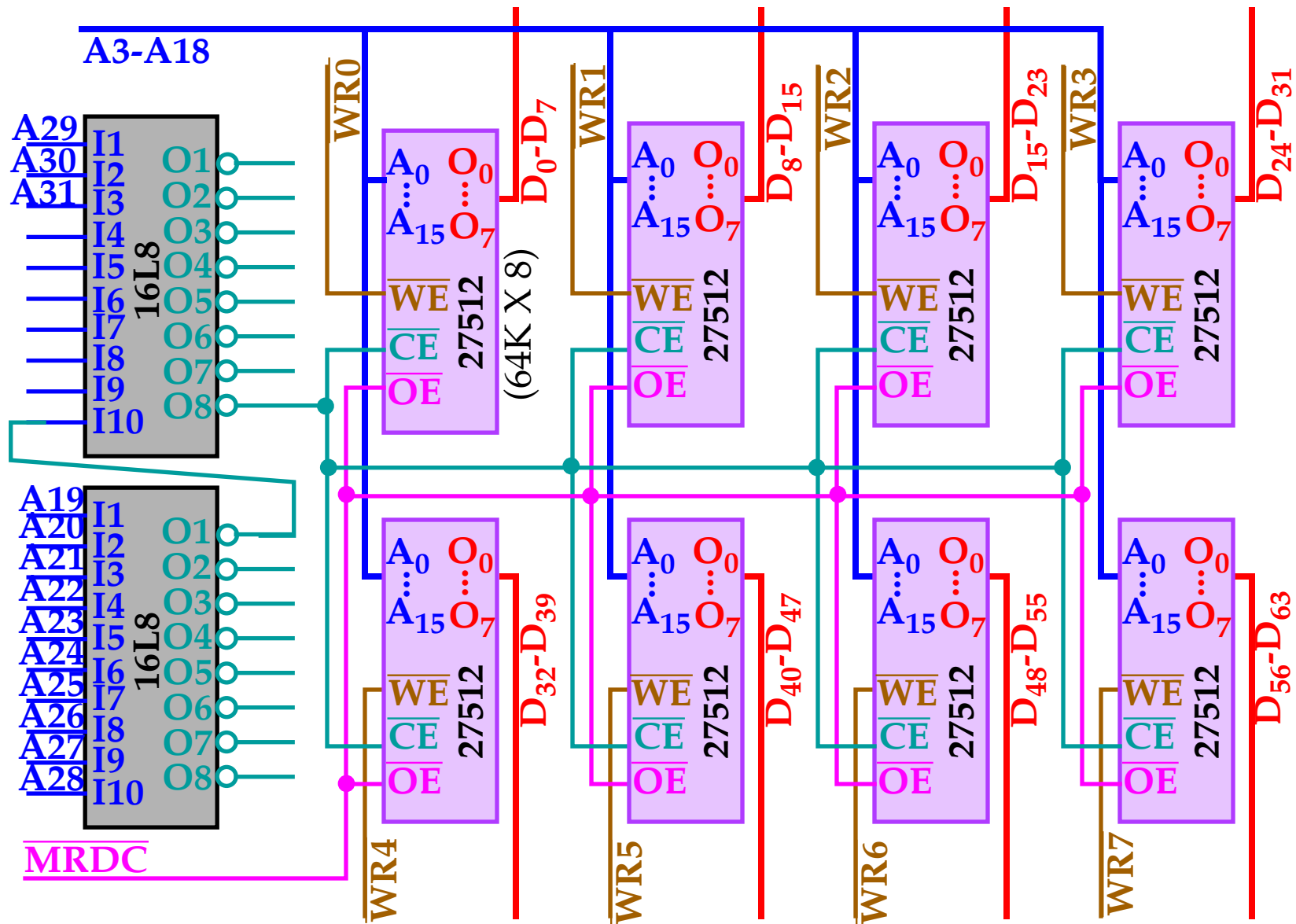

Pentium Memory Interface

 In order to map previous memory into addr. space $FFF80000H-FFFFFFFFH$




;pins 1 2 3 4 5 6 7 8 9 10
A29 A30 A31 NC NC NC NC NC NC GND

;pins 11 12 13 14 15 16 17 18 19 20
U2 CE NC NC NC NC NC NC NC VCC

Equations:
 
$$\overline{CE} = \overline{U2} * A29 * A30 * A31$$



;pins 1 2 3 4 5 6 7 8 9 10
A19 A20 A21 A22 A23 A24 A25 A26 A27 GND

;pins 11 12 13 14 15 16 17 18 19 20
A28 U2 NC NC NC NC NC NC NC VCC

Equations:


$$\overline{U2} = A19 * A20 * A21 * A22 * A23 * A24 * A25 * A26 * A27 * A28$$

Use a 16L8 to do the $\overline{WR0} - \overline{WR7}$ decoding using \overline{MWTC} and $\overline{BE0} - \overline{BE7}$.

See the text -- Figure 10-35.

Memory Architecture

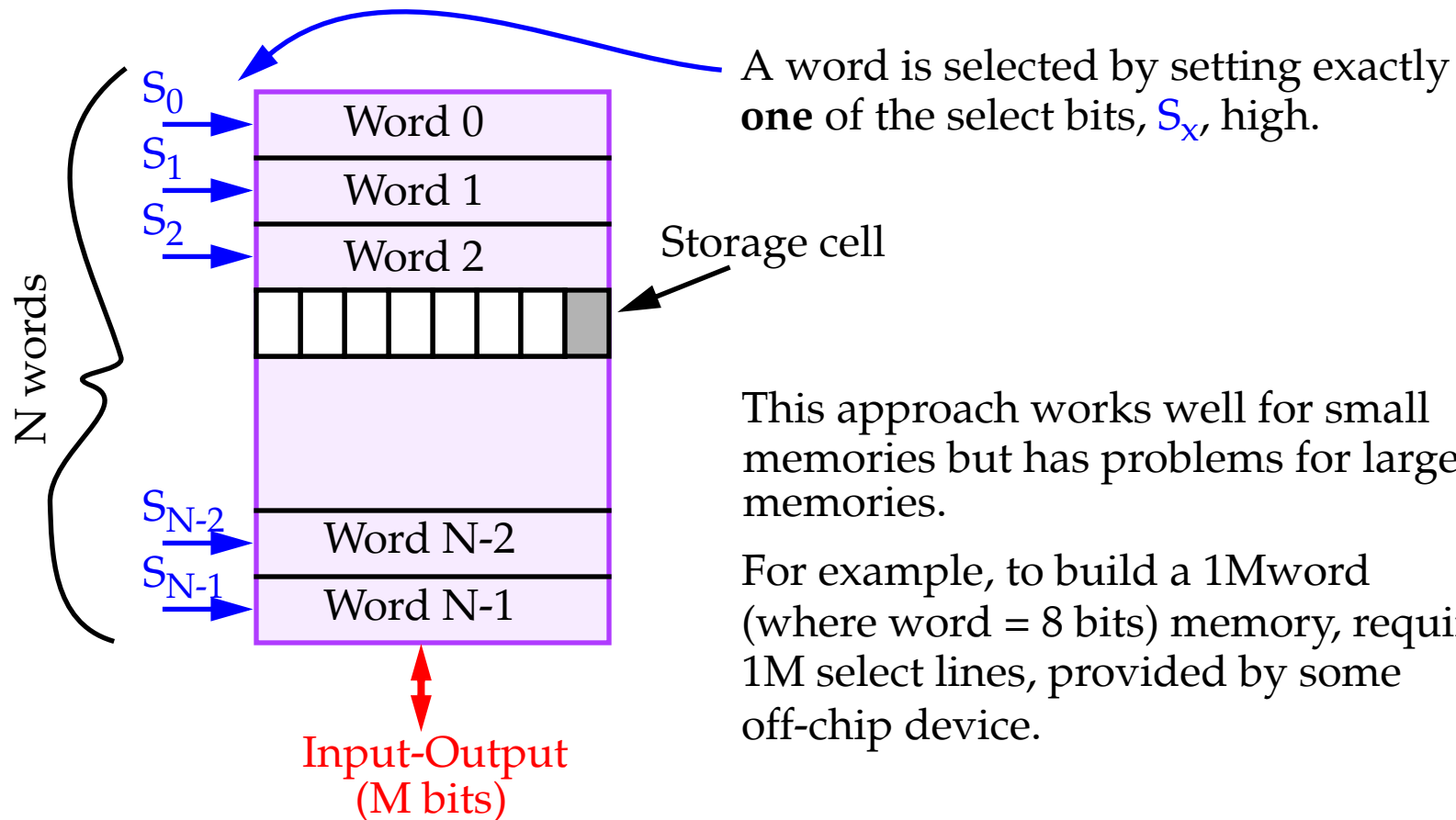
In order to build an N -word memory where each word is M bits wide (typically 1, 4 or 8 bits), a straightforward approach is to stack memory:



This approach is not practical.
What can we do?

Memory Architecture

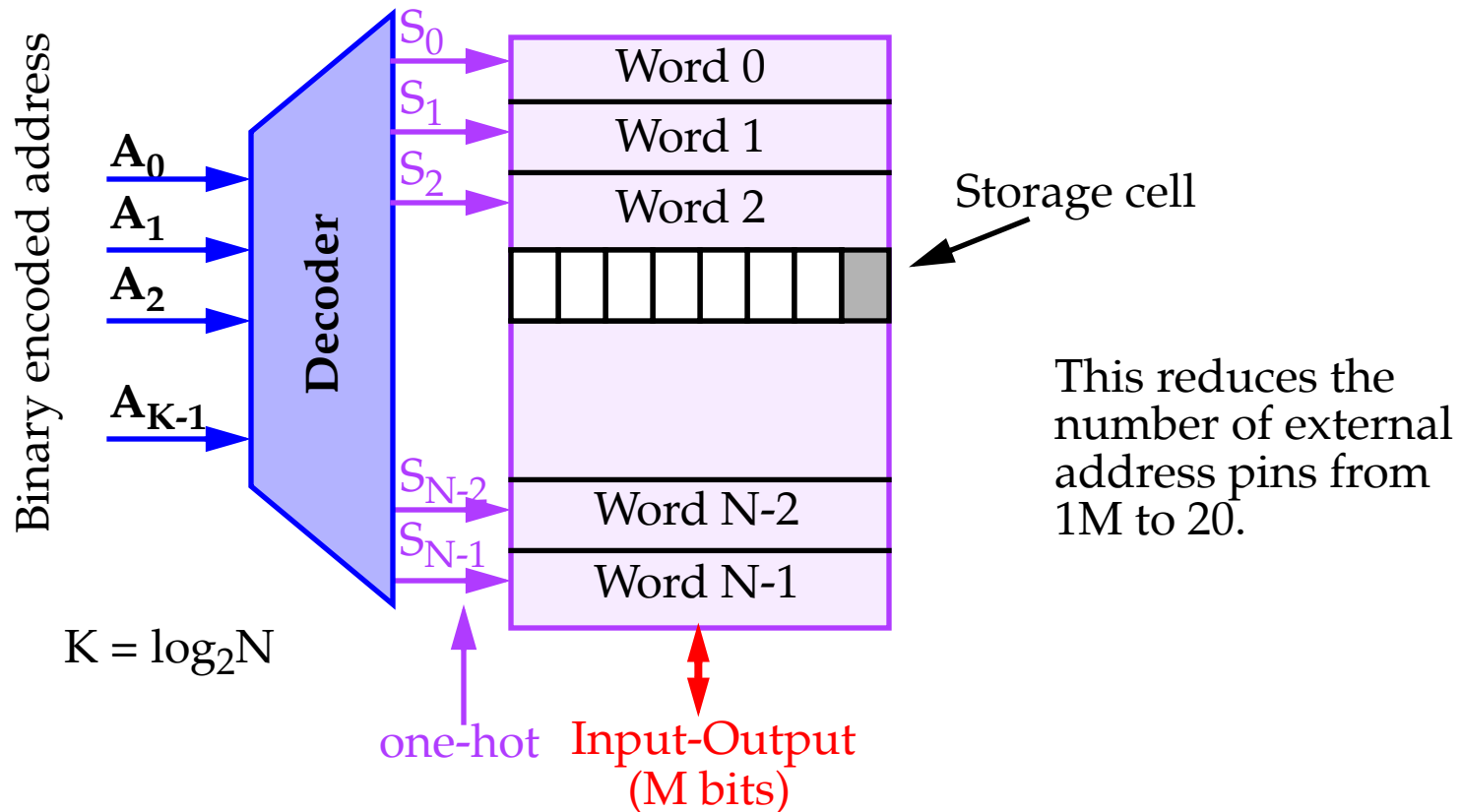Add a decoder to solve the package problem:



This does not address the **memory aspect ratio** problem:

The memory is 128,000 times higher than wide ($2^{20}/2^3$) !

Besides the bizarre shape factor, the design is *extremely slow* since the vertical wires are VERY long (delay is at least linear to length).


Memory Architecture

The vertical and horizontal dimensions are usually very similar, for an aspect ratio of *unity*.

Multiple words are stored in each row and selected simultaneously:

Row address =

A_K to A_{L-1}

 

Column address =

A_0 to A_{K-1}

A column decoder is added to select the desired **word** from a row.


Input-Output
(M bits)

Memory Architecture

This strategy works well for memories up to 64 Kbits to 256 Kbits.

Larger memories start to suffer excess delay along bit and word lines.

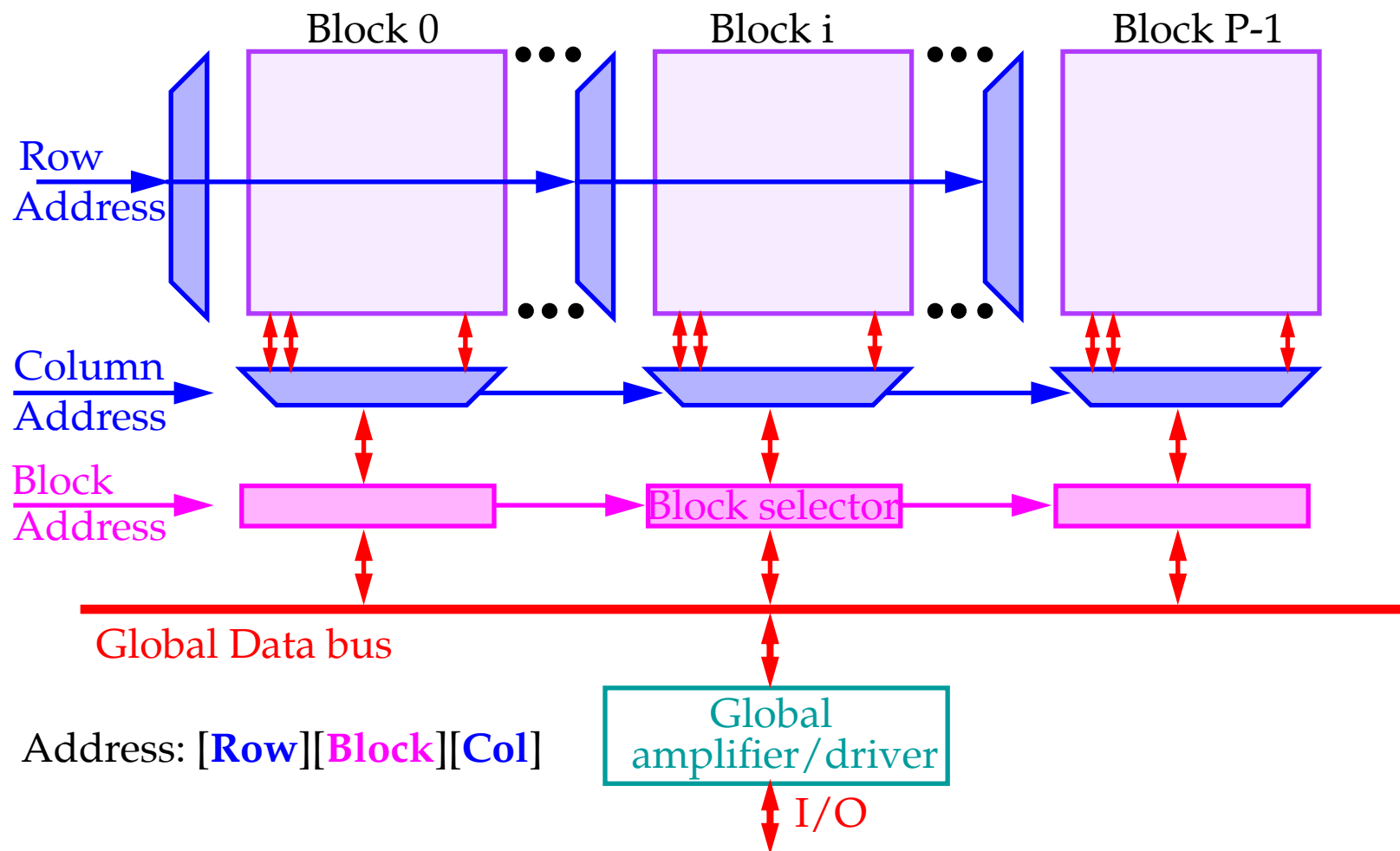A **third dimension** is added to the address space to solve this problem:



Dynamic RAM

DRAM requires refreshing every 2 to 4 *ms*.

Refreshing occurs automatically during a read or write.

Internal circuitry takes care of refreshing cells that are not accessed over this interval.

This special refresh occurs **transparently** while other memory components operate and is called *transparent refresh* or *cycle stealing*.

A $\overline{\text{RAS}}$ -only cycle strobes a row address into the DRAM, obtained by 7- or 8-bit binary counter.


The capacitors are recharged for the selected row by reading the bits out internally and then writing them back.

For a 256K X 1 DRAM with 256 rows, a refresh must occur every 15.6 μs (4ms/256).

For the 8086, a read or write occurs every 800ns.

This allows **19** memory reads/writes per refresh or **5%** of the time.

Dynamic RAM

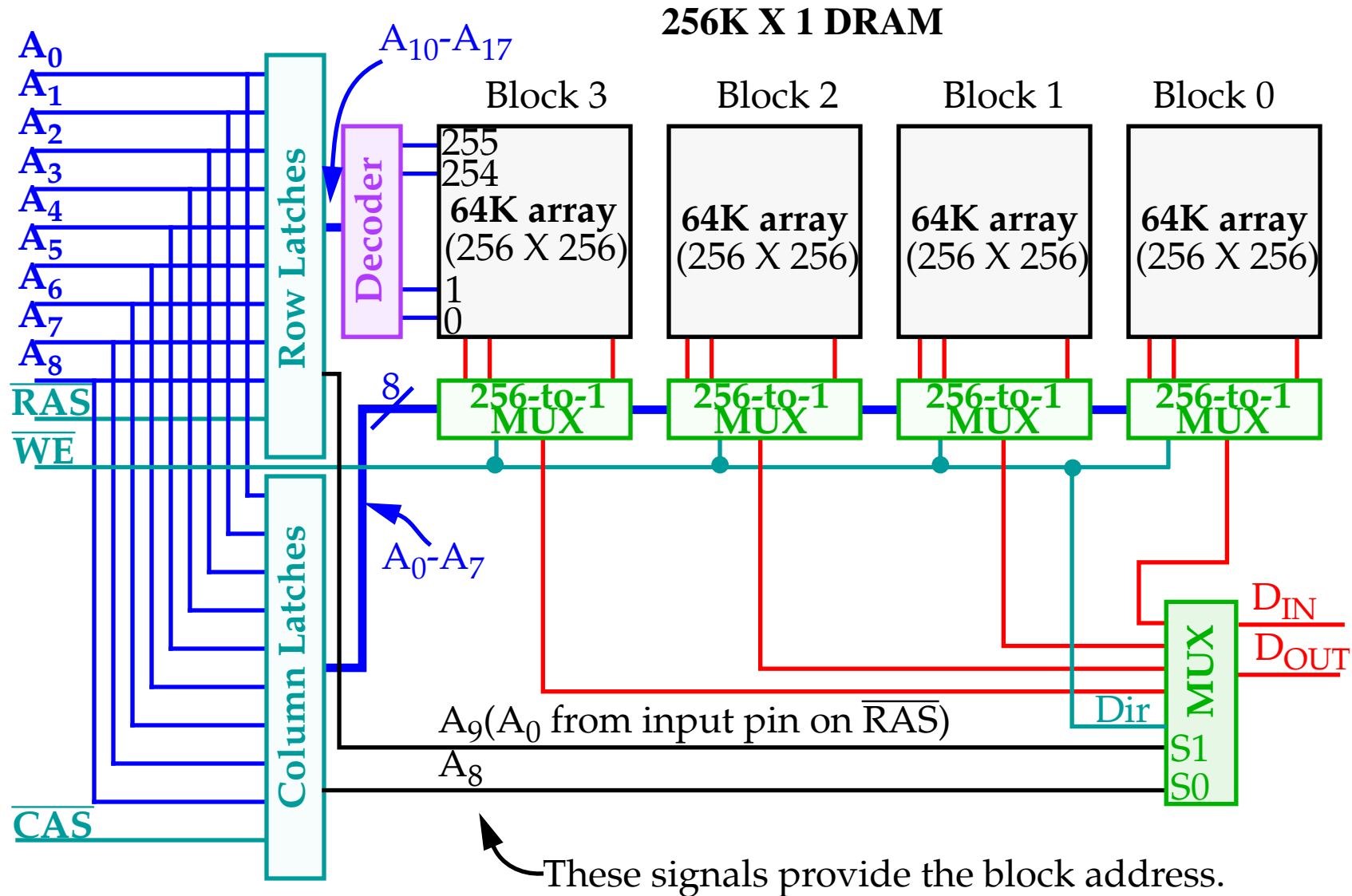

EDO and SDRAM Memory**Extended Data Output memory:**

Any memory access in an **EDO** memory (including a refresh) stores the 256 bits in a set of latches.

Any subsequent access to bytes in this set are **immediately** available (*without the decode time* and therefore wait states).

This works well because of the principle of spatial locality, and improves system performance by 15 to 25 % !

Synchronous Dynamic RAM:

Access times are *10ns* (for use with 66MHz bus) and *8ns* (for use with 100MHz bus).

Standard DRAM access times are *60ns*.

However, these access times *only apply* to the **2nd, 3rd** and **4th 64-bit** reads -- the first takes the same time as a standard DRAM.

EDO and SDRAM Memory**Synchronous Dynamic RAM:**

However, this improves performance again, particularly for reads into cache block sizes of 256 *bits*.

For example, 256 bit transfer takes **three** bus cycles for the *first read* and **three** for the *next three* 64-bit words, for a total of 7 bus cycles.

This contrasts with the 3*4 or 12 bus cycles for DRAM or EDO.

Measurements show about a **10%** increase in performance.

DRAM Controllers:

A DRAM controller is usually responsible for address multiplexing and generation of the DRAM control signals.

These devices tend to get very complex.

We will focus on a simpler device, the *Intel 82C08*, which can control **two** banks of 256K X 16 DRAM memories for a total of 1 MB.

DRAM Controllers:**Intel 82C08:**

Microprocessor bits A_1 through A_{18} (18 bits) drive the 9 **Address Low** (AL) and 9 **Address High** (AH) bits of the 82C08.

9 of each of these are strobed onto the address wires A_0 through A_8 to the memories.


Either RAS0/CAS0 or RAS1/CAS1 are strobed depending on the address.

This drives a *16-bit* word onto the High and Low data buses (if WE is low) or writes an 8 or 16 bit word into the memory otherwise.

WE (from the 82C08), BHE and A_0 are used to determine if a write is to be performed and which byte(s) (low or high or both) is to be written.


Address bit A_{20} through A_{23} along with M/\overline{IO} enable these memories to map onto 1 MByte range (000000H-0FFFFFFH).

DRAM Controllers

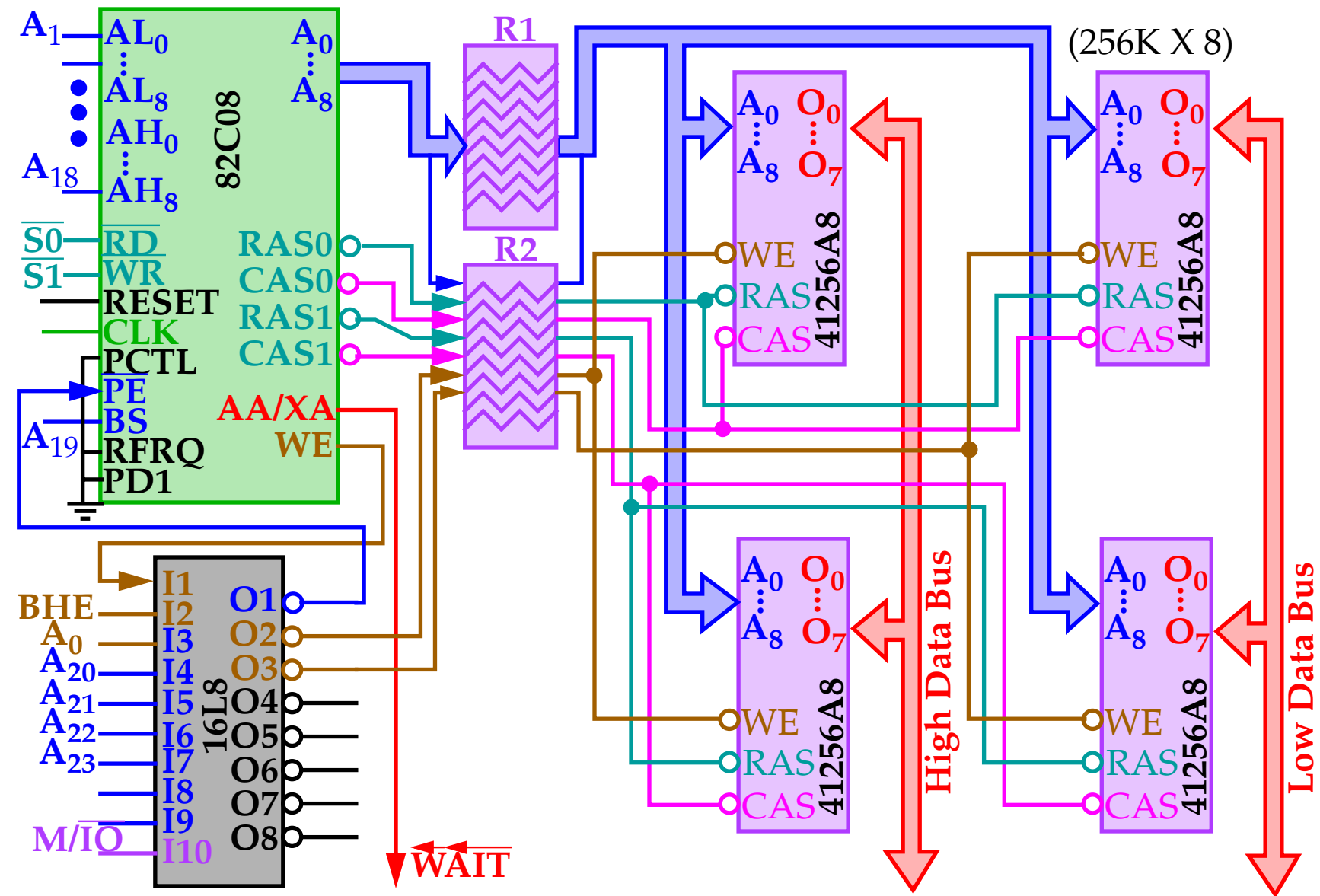

DRAM Controllers:

16L8 Programming:

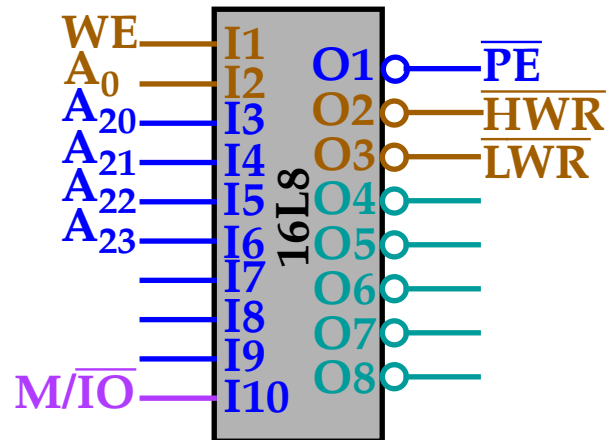

| | | | | | | | | | | |
|------|----|-----|----|-----|-----|-----|-----|----|----|-----|
| pins | 1 | 2 | 3 | 4 | 5 | 6 | 7 | 8 | 9 | 10 |
| | WE | BHE | A0 | A20 | A21 | A22 | A23 | NC | NC | GND |

| | | | | | | | | | | |
|------|-----|----|----|----|----|----|-----|-----|----|-----|
| pins | 11 | 12 | 13 | 14 | 15 | 16 | 17 | 18 | 19 | 20 |
| | MIO | CE | NC | NC | NC | NC | LWR | HWR | PE | VCC |

Equations:

$$/LWR = /A0 * /WE$$

$$/HWR = /BHE * /WE$$

$$/PE = /A20 * /A21 * /A22 * /A23 * MIO$$

