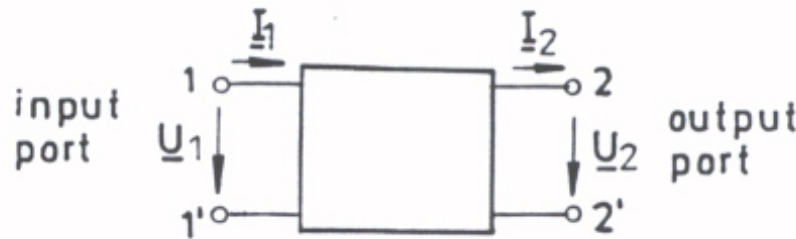


The study of a passive two-port system

Laboratory 20



Port: the current into one of the port terminal is, at every instant of time, equal to the current out of the other terminal of the port (*the port current requirement*).

The fundamental equations. ABCD parameters.

$$\begin{cases} \underline{U}_1 = \underline{A}\underline{U}_2 + \underline{B}\underline{I}_2 \\ \underline{I}_1 = \underline{C}\underline{U}_2 + \underline{D}\underline{I}_2 \end{cases}$$

where $\underline{A}, \underline{B}, \underline{C}, \underline{D}$ are called **fundamental** (or **transmission**) **parameters**
 ($\underline{A}$ and $\underline{D}$ – dimensionless, $\underline{B}$ is impedance, $\underline{D}$ is admittance)

$$\underline{A} = \frac{1}{\left(\frac{\underline{U}_2}{\underline{U}_1} \right)_{\underline{I}_2=0}}$$

- is the reciprocal of the *open-circuit voltage transfer ratio* from port 1 to port 2

$$\underline{B} = \frac{1}{\left(\frac{\underline{I}_2}{\underline{U}_1} \right)_{\underline{U}_2=0}}$$

- is the reciprocal of the *short-circuit transfer admittance* from port 1 to port 2.

$$\underline{C} = \frac{1}{\left(\frac{\underline{U}_2}{\underline{I}_1} \right)_{\underline{I}_2=0}}$$

- is the reciprocal of the *open-circuit transfer impedance* from port 1 to port 2

$$\underline{D} = \frac{1}{\left(\frac{\underline{I}_1}{\underline{I}_2} \right)_{\underline{U}_2=0}}$$

- is the reciprocal of the *short-circuit current transfer ratio* from port 1 to port 2.

Fig. 2-a (Lab book) Determining $\underline{C}$

$$\underline{C} = \frac{\underline{I}_1}{\underline{U}_2} = \frac{I_1 \cdot e^{j\varphi_{I1}}}{U_2 \cdot e^{j\varphi_{U2}}} = \underbrace{\frac{I_1}{U_2}}_C \cdot e^{\frac{j(\varphi_{I1} - \varphi_{U2})}{\varphi_C}}$$

Where

C – the modulus of the constant $\underline{C}$

φ_C – the phase of the constant $\underline{C}$

We measured: I_1 ; $U_2=V$; $P=U_2 \cdot I_1 \cdot \cos \varphi_C$

Compute: $C = \frac{I_1}{U_2}$ and $\cos \varphi_C = \frac{P}{U_2 \cdot I_1}$

Fig. 2-b (Lab book) Determining A

$$\underline{A} = \frac{\underline{U}_1}{\underline{U}_2} = \frac{U_1 \cdot e^{j\varphi_{U1}}}{U_2 \cdot e^{j\varphi_{U2}}} = \underbrace{\frac{U_1}{U_2}}_A \cdot e^{\underbrace{j(\varphi_{U1}-\varphi_{U2})}_{\varphi_A}}$$

Where

A – the modulus of the constant A

φ_A – the phase of the constant A

We measured: $U_1=$; $U_2=$; $I_R=$; $P=U_2 \cdot I_R \cdot \cos \varphi_A$

Compute A and φ_A .

Fig. 2-c (Lab book) Determining B

$$\underline{B} = \frac{\underline{U}_1}{\underline{I}_2} = \frac{U_1 \cdot e^{j\varphi_{U1}}}{I_2 \cdot e^{j\varphi_{I2}}} = \underbrace{\frac{U_1}{I_2}}_B \cdot e^{\underbrace{j(\varphi_{U1} - \varphi_{I2})}_{\varphi_B}}$$

Where

B – the modulus of the constant B

φ_B – the phase of the constant B

We measured: $U_1=$; $I_2=$; $P=U_1 \cdot I_2 \cdot \cos \varphi_B$

Compute B and φ_B .

Fig. 2-d (Lab book) Determining D

$$\underline{D} = \frac{\underline{I}_1}{\underline{I}_2} = \frac{I_1 \cdot e^{j\varphi_{I1}}}{I_2 \cdot e^{j\varphi_{I2}}} = \underbrace{\frac{I_1}{I_2}}_{\underline{D}} \cdot e^{\frac{j(\varphi_{I1} - \varphi_{I2})}{\varphi_D}}$$

Where

$\underline{D}$ – the modulus of the constant D

φ_D – the phase of the constant D

We measured: $I_1=$; $I_2=$; $U_R=$; $P=U_R \cdot I_2 \cdot \cos \varphi_D$

Compute $\underline{D}$ and φ_D .

Fig. 3 (Lab book) Determining $\underline{Z}$

$$\underline{Z}_{10} = \frac{\underline{U}_{10}}{\underline{I}_{10}} = \frac{U_{10} \cdot e^{j\varphi_{U10}}}{I_{10} \cdot e^{j\varphi_{I10}}} = \frac{U_{10}}{\underbrace{I_{10}}_{Z_{10}}} \cdot e^{\frac{j(\varphi_{U10} - \varphi_{I10})}{\varphi_{Z10}}}$$

We measured:

$$\begin{aligned} I_{10} &=; & U_{10} &=; & P_{10} &= U_{10} \cdot I_{10} \cdot \cos \varphi_{10} = \\ I_{1sc} &=; & U_{1sc} &=; & P_{1sc} &= U_{1sc} \cdot I_{1sc} \cdot \cos \varphi_{1sc} = \\ I_{20} &=; & U_{20} &=; & P_{20} &= U_{20} \cdot I_{20} \cdot \cos \varphi_{20} = \\ I_{2sc} &= 0,36A; & U_{2sc} &=; & P_{2sc} &= U_{2sc} \cdot I_{2sc} \cdot \cos \varphi_{2sc} = \end{aligned}$$

Compute: Z_{10} and φ_{10} ; Z_{1sc} and φ_{1sc} ; Z_{20} and φ_{20} ; Z_{2sc} and φ_{2sc}